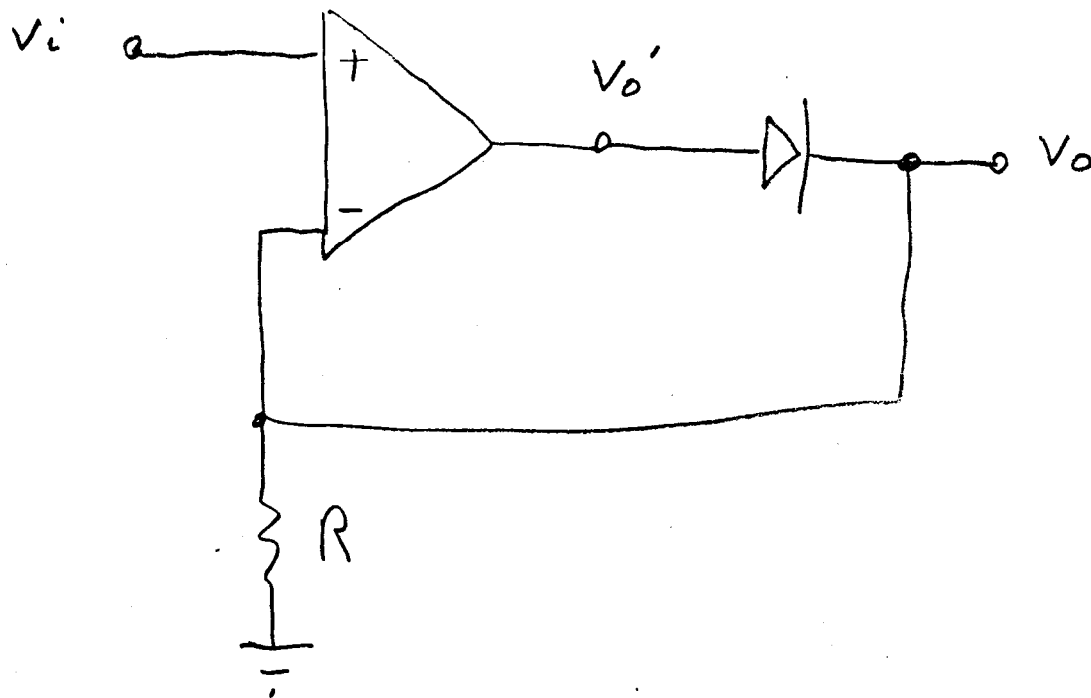



$V_r \equiv$ on voltage $\approx 0.65V$

Precision Half Wave Rectifier



$V_i > 0 \quad \text{E} \quad V_o' > V_r$


Diode Forward Biased

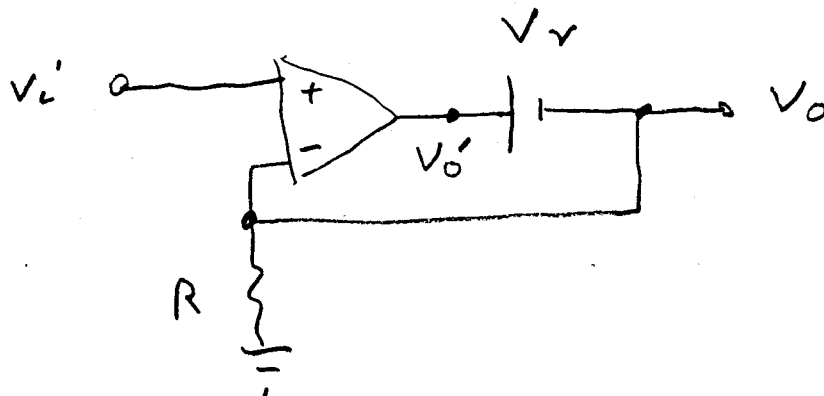

$V_o = V_i$
 $V_o' = V_o + V_r$


$V_i < 0$

Diode Reverse Biased

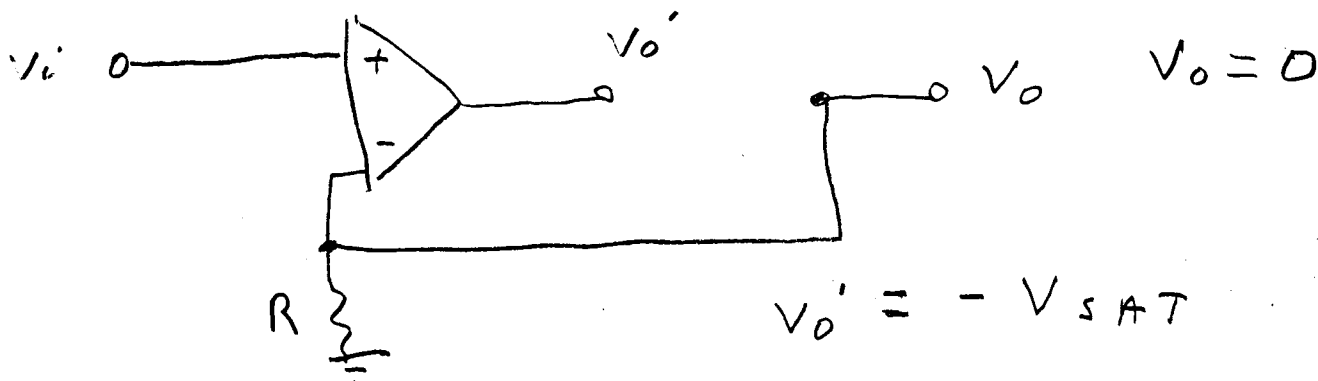

$V_o = 0$
 $V_o' = -V_{SAT}$


Improved Precision Half Wave Rectifier

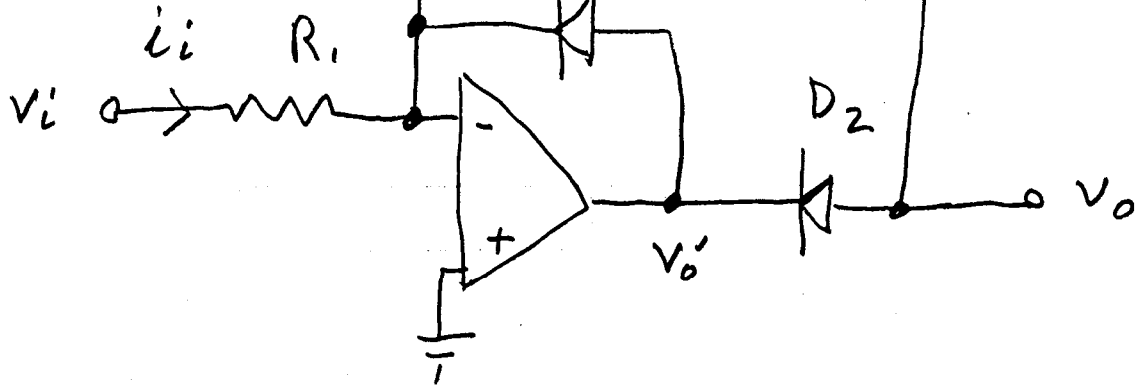

$V_i > 0$

$V_{o'} < V_r$

D_1 reverse
 D_2 forward

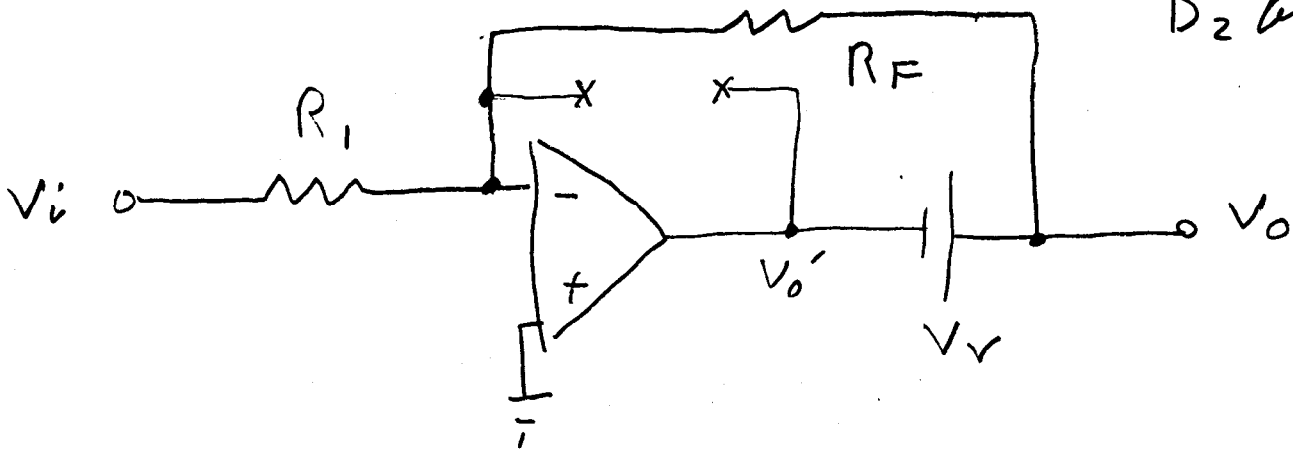


$V_o = - \frac{R_F}{R_i} V_i$

$V_{o'} = V_o - V_r$

$V_i < 0$


$V_{o'} > V_r$

D_1 forward
 D_2 reverse

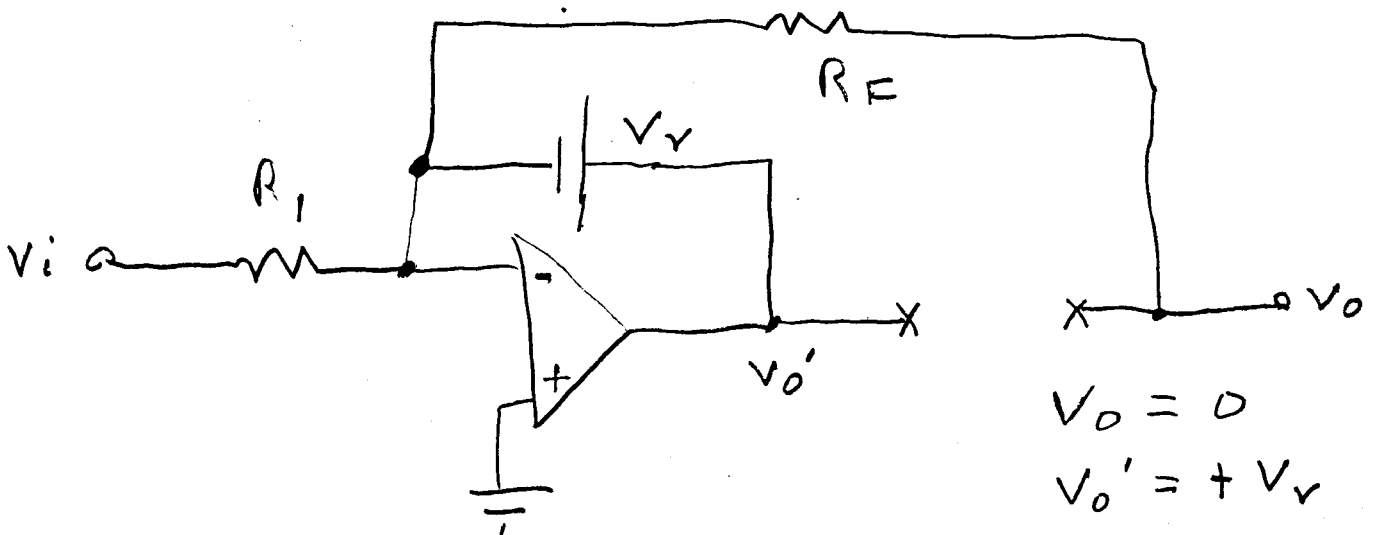

$V_o = 0$

$V_{o'} = +V_r$

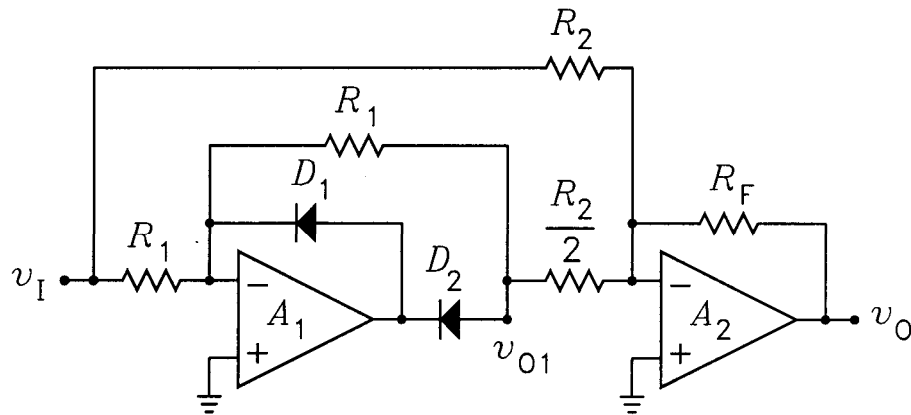

First Precision Full Wave Rectifier

$v_i > 0$ D_1 off D_2 on

$$v_{O1} = - \frac{R_1}{R_1} v_i = -v_i$$

$$v_o = - \frac{R_F}{R_2} v_i - \frac{R_F}{\frac{R_2}{2}} v_{O1} = - \frac{R_F}{R_2} v_i - \frac{2 R_F}{R_2} (-v_i)$$


$$v_o = \frac{R_F}{R_2} v_i$$

$v_i < 0$ D_1 on D_2 off $v_{O1} = 0$

$$v_o = - \frac{R_F}{R_2} v_i$$

$$v_o = \frac{R_F}{R_2} |v_i|$$

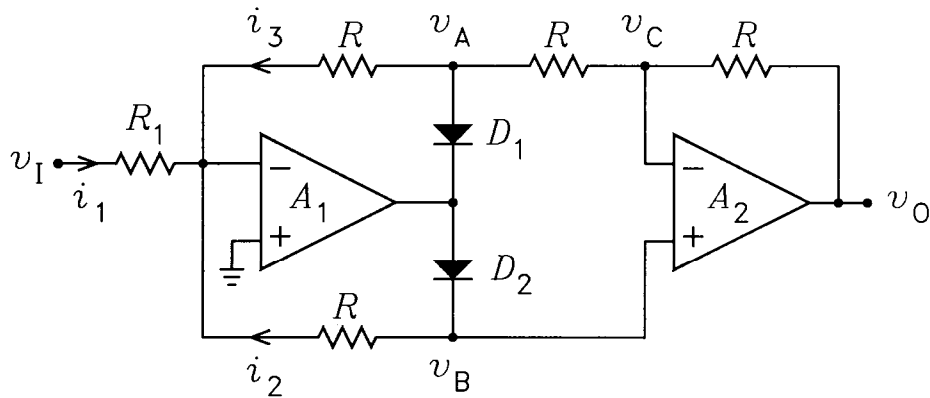Absolute Value
Circuit or Full
Wave Rectifier



Second Precision Full Wave Rectifier

$v_i > 0$ D_1 on D_2 off

$$i_2 = 0 \quad v_0 = -\frac{R}{R} v_A \quad v_A = -\frac{R}{R_1} v_i$$

$$v_0 = \frac{R}{R_1} v_i$$

$v_i < 0$ D_1 off D_2 on


$$v_0 = \left[1 + \frac{R}{2R} \right] v_B = \frac{3}{2} v_B$$

$$v_B = -\frac{R \parallel (2R)}{R_1} v_i = -\frac{2}{3} \frac{R}{R_1} v_i$$

$$v_0 = -\frac{R}{R_1} v_i$$

$$v_0 = \frac{R}{R_1} |v_i|$$

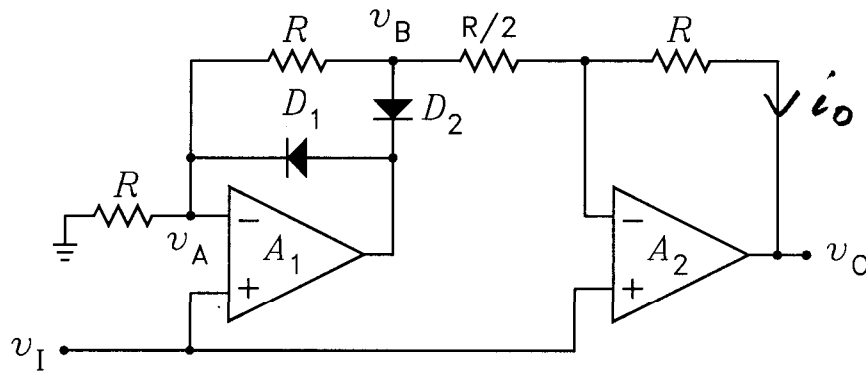absolute value
circuit or full
wave rectifier



Third Precision Full Wave Rectifier

$v_i > 0$ D_1 on D_2 off

$i_o = 0$ $v_o = v_i$


$v_i < 0$ D_1 off D_2 on

$$v_B = 2v_i$$

$$i_o = \frac{v_B - v_i}{\frac{R}{2}} = \frac{2v_i}{R}$$

$$v_o = v_i - i_o R = v_i - 2v_i = -v_i$$

$v_o = |v_i|$ Absolute Value
Circuit or Full Wave
Rectifier

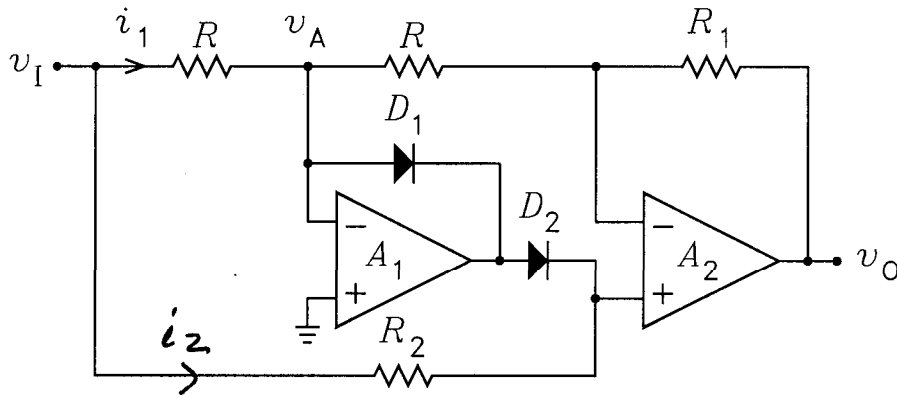

Fourth Precision Full Wave Rectifier

$v_i > 0$ D_1 on D_2 off

$$i_2 = 0$$

$$v_o = \left[1 + \frac{R_1}{R} \right] v_i$$

$v_i < 0$ D_1 off D_2 on

$$i_1 = \frac{v_i}{R}$$


$$v_o = -i_1 [R + R_1] = -\frac{R + R_1}{R} v_i$$

$$v_o = -\left[1 + \frac{R_1}{R} \right] v_i$$


$$v_o = \left[1 + \frac{R_1}{R} \right] |v_i|$$

absolute value
circuit or
full wave
rectifier

Peak Hold Circuit

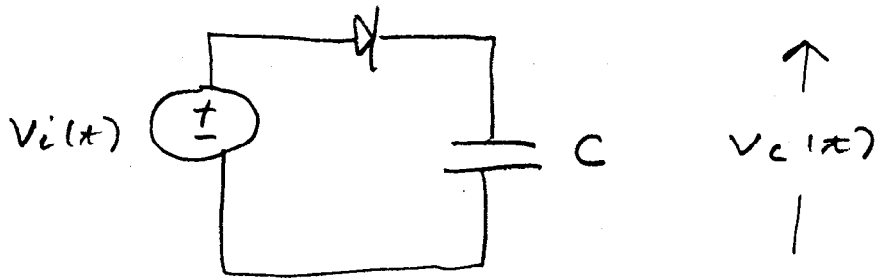

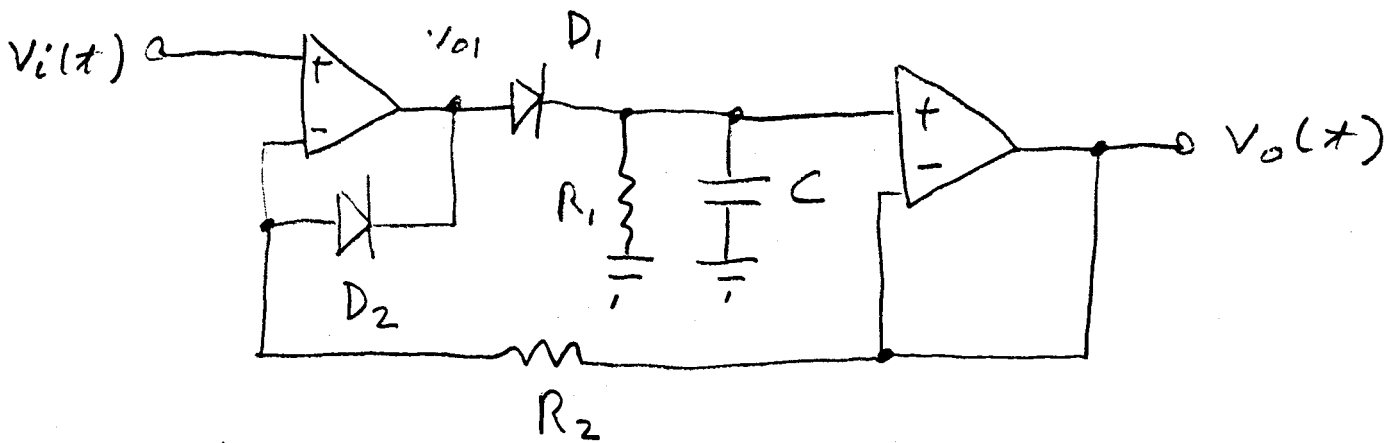
If diode is ideal $V_o(t)$ is a constant equal to the peak value of $V_i(t)$. It would hold it forever.



If $R_1 = \infty$ $V_o(t)$ is the peak of $V_i(t)$

For peak tracking pick

$\tau = R_1 C$ to be a few seconds.

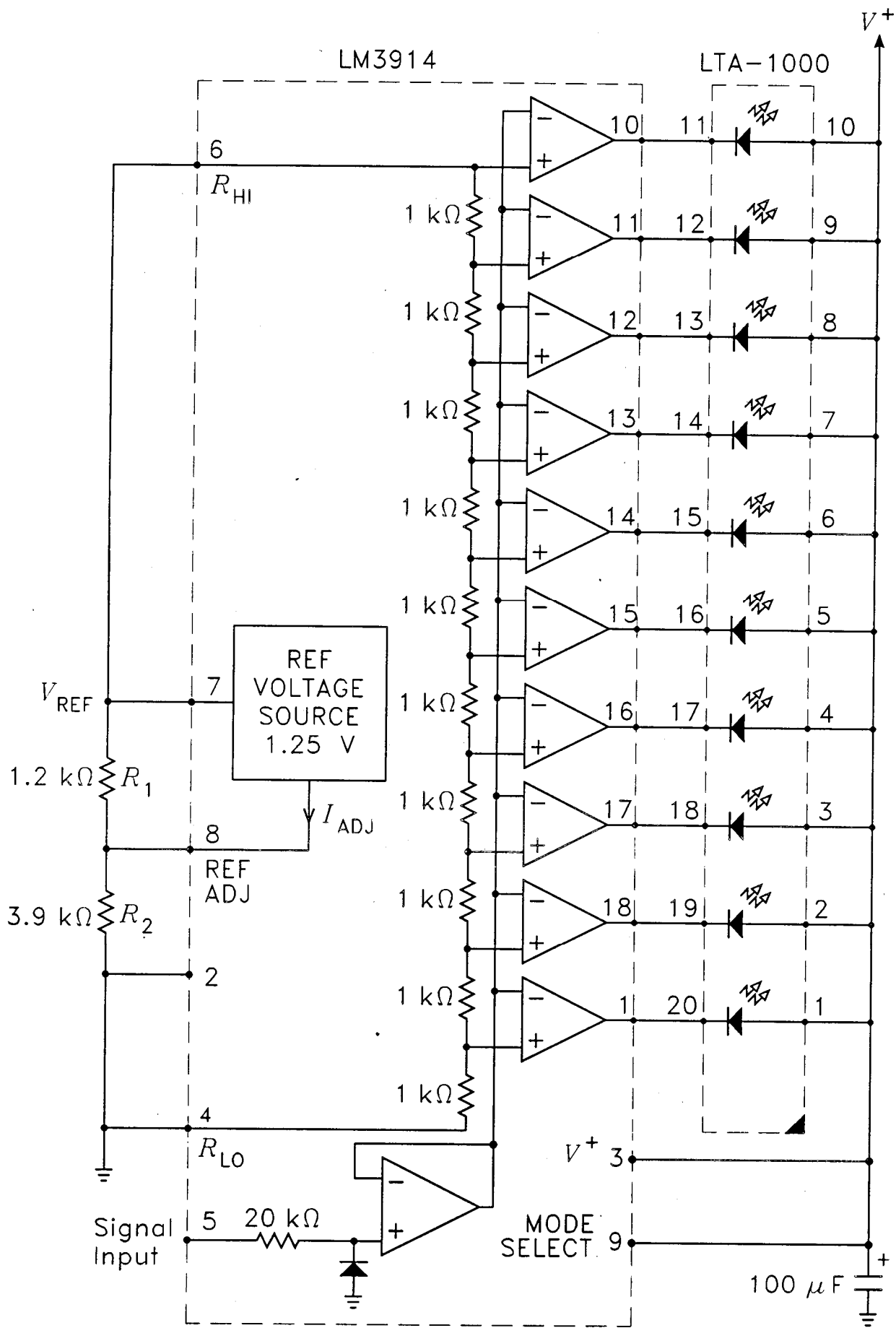

Georgia Institute of Technology

School of Electrical and Computer Engineering

ECE 3042

Microelectronic Circuits Laboratory

Verification Sheet

NAME: _____

SECTION: _____

GT NUMBER: _____

GTID: _____

Experiment 5: Non-Linear Op-Amp Circuits

Procedure	Time Completed	Date Completed	Verification (Must demonstrate circuit)	Points Possible	Points Received
2. Half-Wave Rectifiers				30	
3. Full-Wave Rectifier *(See Table Below)				10	
4. Peak Hold Circuit				10	
5. Bar-Graph Array				10	
6. Level Indicator *(See Table Below)				40	

* Build only one of the full-wave rectifier circuits shown in the lab manual. From the table below, determine which full-wave rectifier circuit to build and the input voltage for the level indicator.

Last Digit of GTID	0,1,2	3,4,5	6,7	8,9
FWR Circuit	1	2	3	4
Input Voltage for Level Indicator	1 Vrms	2 Vrms	3 Vrms	5 Vrms

To be permitted to complete the experiment during the open lab hours, you must complete at least **four** procedures during your scheduled lab period or spend your entire scheduled lab session attempting to do so. A signature below by your lab instructor, Dr. Brewer, or Dr. Robinson permits you to attend the open lab hours to complete the experiment and receive full credit on the report. Without this signature, you may use the open lab to perform the experiment at a 50% penalty.

SIGNATURE: _____

DATE: _____

ECE 3042 Check-off Requirements for Experiment 5

Make sure you have made all required measurements before requesting a check-off. For all check-offs, you must demonstrate the circuit or measurement to a lab instructor. All screen captures must have a time/date stamp.

2. Half-Wave Rectifiers

- ✓ Screen captures displaying input and output of the three rectifiers for 100Hz, 10kHz, and 100kHz input frequencies. Show measured V_{pp} for each channel.
- ✓ Screen captures displaying XY plots of the three rectifiers for 100 Hz, 10kHz, and 100kHz input frequencies.

3. Full-Wave Rectifier

- ✓ Screen capture displaying input and output of rectifier for 100Hz input frequency. Show measured V_{pp} for each channel.
- ✓ Screen capture displaying XY plot of rectifier for 100 Hz input frequency.

4. Peak-Hold Circuit

- ✓ Screen capture displaying input sine wave and output dc voltage. Make sure the volts per division settings are the same for both channels and that both channels are dc coupled. Also set the ground level for both channels to be the same (use the vertical position control to place the ground level indicators on the left side of the scope trace on top of each other).
- ✓ Description of how the output responds as the input is varied both up and down.
- ✓ Answer to question: Why does the output voltage go up faster than it goes down?
- ✓ Retain this circuit for possible use in procedure 6.

5. Bar-Graph Array

- Note that there is a 10k pot and a fixed 10k resistor in the circuit of Fig. 5.10. The wiper of the pot connects to pin 5 of the bar graph display. The dmm is connected between pin 5 and ground to measure the dc voltage.
- ✓ Table of voltages at which each LED in the array lights.

6. Level Indicator

- ✓ Demonstration of designed circuit. The last LED must just turn on for the input voltage found from the table on the verification sheet. Remember, the voltage at pin 5 must be a dc voltage but the input signal is a sinusoid.
- ✓ Schematic of designed circuit.