

ECE 3042 Lecture Exam No. 2 Spring 2013

FRIDAY, MARCH 15, 4-5 PM


AD LOGON _____

Name _____

Key

Closed Book and Note. Calculator Permitted. Four Equally Weighted Problems. All Work Must Be Shown for Credit. Box All Answers.

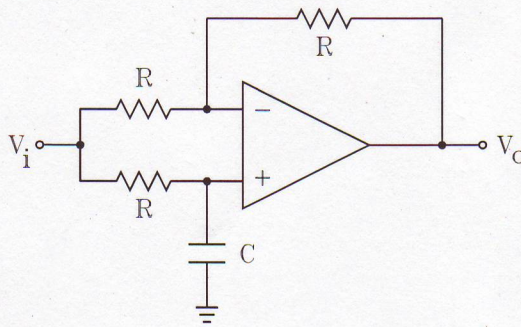1. The component values for the filter shown below are $R = 8 \text{ k}\Omega$, $C = 5 \text{ nF}$, and the op amp may be considered to be ideal.



- 2 What is the order of the filter? 1, One, Unity
- 2 What type of filter is it? All Pass
- 2 What is the linear dc gain? 1
- 2 What is the linear infinite frequency gain? -1 (Accept +1)
- 2 What is the gain in dB when $f = 7.3 \text{ kHz}$? 0
- 2 What is the phase shift in degrees when $f = 7.3 \text{ kHz}$? -123°

Derive the complex transfer function $T(s) = V_o(s)/V_i(s)$. Express the answer in terms of the symbols s , R , and C (not the numerical values).

$$5 \quad V_o = -\frac{R}{R} V_i + \frac{\frac{1}{sC}}{R + \frac{1}{sC}} \left[1 + \frac{R}{R}\right] V_i$$

$$\frac{V_o}{V_i} = -1 + \frac{2}{1 + 2RC} = \frac{1 - 2RC}{1 + 2RC}$$

8 try

2. A certain filter has the complex transfer function

$$T(s) = K \frac{\left(\frac{s}{\omega_o}\right)^2 - \frac{1}{Q} \frac{s}{\omega_o} + 1}{\left(\frac{s}{\omega_o}\right)^2 + \frac{1}{Q} \frac{s}{\omega_o} + 1}$$

where $K = 8$, $f_o = 73$ kHz, and $Q = 10$.


- 3 What is the order of the filter? 2, Two, Second
- 3 What type of filter is it? All Pass
- 3 What is the dc phase shift? 0°
- 3 What is the linear dc gain? 8
- 3 What is the linear infinite frequency gain? 8
- 3 What is the gain in dB when $f = 43$ kHz? 18.1 dB
- 3 What is the phase shift in degrees when $f = 43$ kHz? -10.3°

$$T(j43 \text{ kHz}) = 8 \frac{\left(j \frac{43}{73}\right)^2 - \frac{1}{10} \left(j \frac{43}{73}\right) + 1}{\left(j \frac{43}{73}\right)^2 + \frac{1}{10} \left(j \frac{43}{73}\right) + 1} =$$

$$8 \angle -10.308^\circ$$

y try

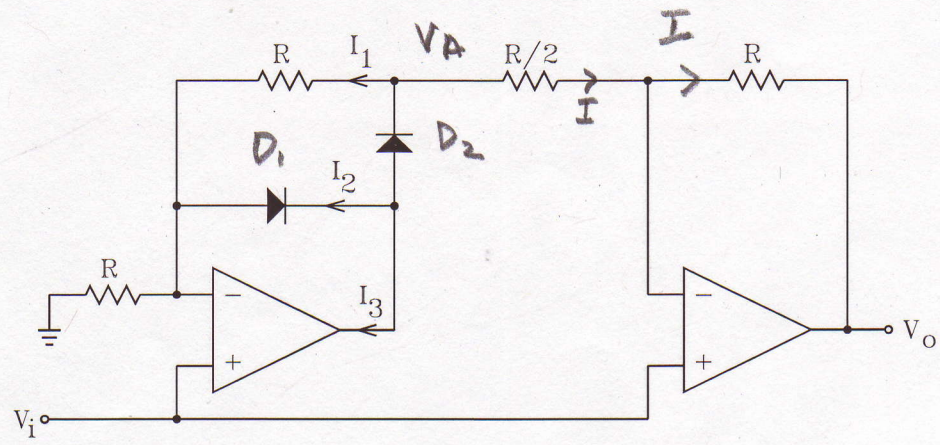3. In the circuit shown below the op amps may be considered ideal excepts that they have an upper and lower saturation voltage of ± 15 V. The resistor value is $R = 2\text{ k}\Omega$. The diodes are semiconductor diodes with an on voltage of 0.65 V. Complete the table.




V_i	I_1	I_2	I_3	V_o
-3V	0	-1.5 mA	1.5 mA	-3
0V	0	0	0	0
3V	1.5 mA	0	-4.5 mA	-3

2 each

$V_i < 0$ D_1 on D_2 off
 $I_1 = 0$ $V_o = V_i$ $I_2 = -\frac{3}{2} \text{ mA}$
 $I_3 = -I_2 = \frac{3}{2} \text{ mA}$

$V_i > 0$ D_1 off D_2 on
 $I_1 = \frac{3}{2} \text{ mA}$ $V_o = V_i$ $V_A = 2V_i$
 $I = \frac{2V_i - V_i}{R/2} = \frac{6 - 3}{1} = 3 \text{ mA}$ $V_o = V_i - RI = 3 - 2 \cdot 3 = -3 \text{ V}$
 $I_3 = -(I_1 + I) = -(1.5 + 3) = -4.5 \text{ mA}$
 1 try

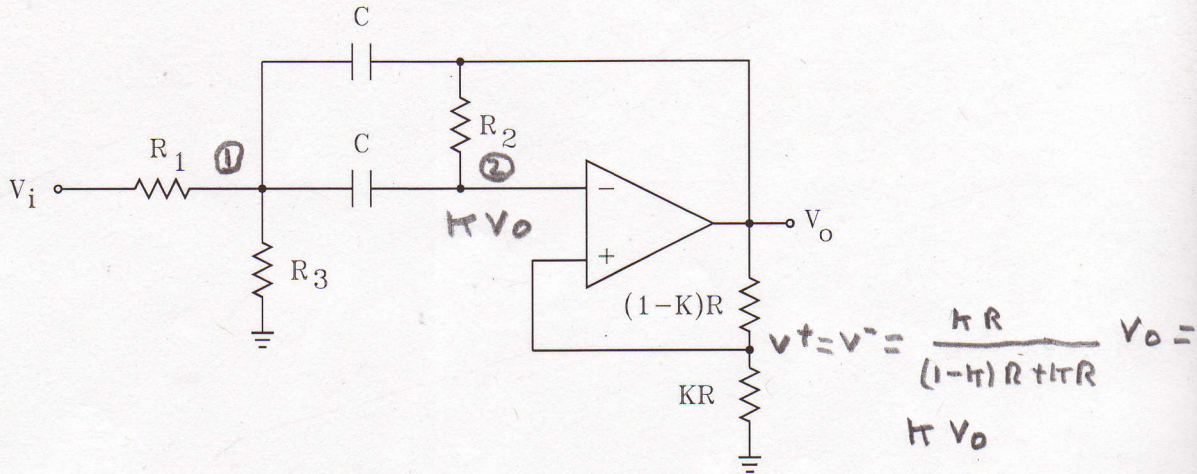4. The op amp in the filter circuit shown below may be considered to be ideal.



What is the order of the filter? 2, Two, Second 4
 What type of filter is it? Band Pass 4
 What is the linear dc gain? 0 4
 What is the linear infinite frequency gain? 0 4

Derive the complex transfer function $T(s) = V_o(s)/V_i(s)$. Express the answer in terms of the symbols s, R_1, R_2, R_3, C , and the parameter K . (K is just a parameter that varies from 0 to 1, viz. the load resistor is a pot)

KCL @ node 1 5

$$\frac{V_i - V_1}{R_1} + sC[V_o - V_1] + sC[KV_o - V_1] - \frac{V_1}{R_3} = 0 \quad \left. \begin{array}{l} \text{simultaneous} \\ \text{solution} \end{array} \right\}$$

KCL @ node 2 $sC[V_1 - KV_o] = [KV_o - V_o]/R_2 \Rightarrow$

$$T(s) = KV_o \frac{\frac{1}{Q} \frac{s}{\omega_0}}{\left(\frac{s}{\omega_0}\right)^2 + \frac{1}{Q} \frac{s}{\omega_0} + 1}$$

$$\omega_0 = \frac{\sqrt{1 + \frac{R_1}{R_3}}}{C \sqrt{R_1 R_2}}$$

$$Q = \frac{\sqrt{1 + \frac{R_1}{R_3}}}{2 \sqrt{\frac{R_1}{R_2}} - \frac{K}{1-K} \sqrt{\frac{R_2}{R_1}} \left[1 + \frac{R_1}{R_3}\right]}$$

$$KV_0 = \frac{1}{K \left[1 + \frac{R_1}{R_3}\right] - 2 \frac{R_1}{R_2} (1-K)} \quad 4$$

ECE 3042 Lecture Exam 2 Spring 2013 March 15 4-5pm

