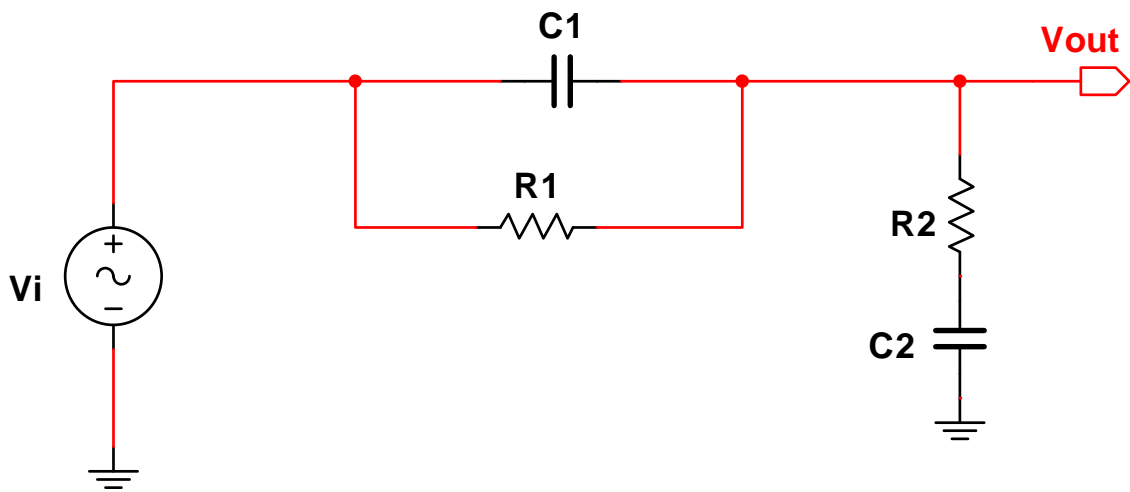


ECE 3043 Spring 2020
Homework Problem Set No 1 for Experiment No. 2

Due Week of January 20



1. For the circuit shown above derive the complex transfer function $H(s) = V_o/V_i$. Express it as a function of the symbols for the resistors and capacitor and the complex frequency variable s . Simplify it as a ratio of two first order polynomials in s

$$H(s) = K \frac{1 + s\tau_z}{1 + s\tau_p} \quad (1)$$

2. Plot the Bode plot for the circuit using either Mathcad or Matlab. Plot the frequency from $f = 1$ Hz to 1 MHz Plot the magnitude in dB and the phase in degrees. The values of the circuit components are $R_1 = 100$ k Ω , $R_2 = 1$ k Ω , $C_1 = 1$ nF, and $C_2 = 0.1$ μ F. Make the same plot as in Problem 2 using National Instruments SPICE (Multisim).
3. Make the same plot as in Problem 2 using National Instruments SPICE (Multisim).
4. Does anything unusual happen in the frequency response plot occur when $f = 1/(2\pi\sqrt{R_1R_2C_1C_2})$? If so describe it.