

# ECE 3043 Spring 2020

## Homework Problem Set No. 4 for Experiment No. 4

Due Week of February 10

1. For the circuit shown below, use National Instruments SPICE (Multisim) to plot the Bode plot of the complex transfer function  $V_o/V_i$ , as the frequency of the voltage source,  $v_i(t)$ , varies from  $0.1f_o$  to  $10f_o$ . where  $f_o$  is the resonant frequency of the circuit. Compare the simulation results with the theoretical results for  $f_o$ ,  $Q$ , and  $\Delta f$ . Assume that the voltage source  $v_i(t)$  is a sine wave with an rms value of 1 V. The component values are  $R_1 = 20 \text{ k}\Omega$ ,  $R_2 = 20 \text{ k}\Omega$ ,  $L = 3 \text{ mH}$ , and  $C = 1 \text{ nF}$ . Use either Mathcad and Matlab to plot the magnitude and phase of the voltage  $v_o(t)$ ; assume that the phase of the source  $v_i(t)$  is zero with the positive side up. (Note that since the input is unity this is equivalent to finding the Bode plot.)
2. For the circuit shown below plot  $v_o(t)$  versus  $t$  using either MathCad or Matlab. The range of  $t$  for the plot is from 0 to  $4T_d$  where  $T_d = 1/f_d$ ,  $f_d = f_o\sqrt{1-\zeta^2}$ ,  $\zeta = (G/2)\sqrt{L/C}$  and  $G = 1/R$  where  $R$  is the Norton resistance seen by the parallel combination of  $L$  and  $C$ . The input is  $v_i(t) = E_o u(t)$  where  $E_o = 10 \text{ V}$  and  $u(t)$  is the unit step function. Compare the theoretical and simulation results for the driven frequency,  $f_d$ , and the attenuation factor of the envelope,  $\alpha$ , (use the  $i_c(t)$  plot for this with Multisim). The component values are the same as for Problem 1.

