

# Georgia Institute of Technology

College of Engineering

School of Electrical and Computer Engineering

ECE 6416: Low-Noise Electronic Circuit Design

Fall Semester 430 BC

Date Performed: September 22, 430 BC

Date Submitted: October 28, 430 BC



Percival Heathcliff Pythagoras

AD Login: pt345

## Objective

The objective of this experiment is to design, simulate, evaluate experimentally and document a low-noise amplifier circuit. The equivalent input noise of the amplifier is to be minimized.

## Target Design

### Part 1: Circuit Topology

Figure 1 below shows the topology of the target circuit to be used for designing the low-noise amplifier. It consists of a common-emitter (CE) common-base (CB) cascode pair as the amplifier stage to provide voltage gain, followed by a DC-coupled common-collector (CC) low-impedance output stage. BJTs are intended to be used as the active devices.

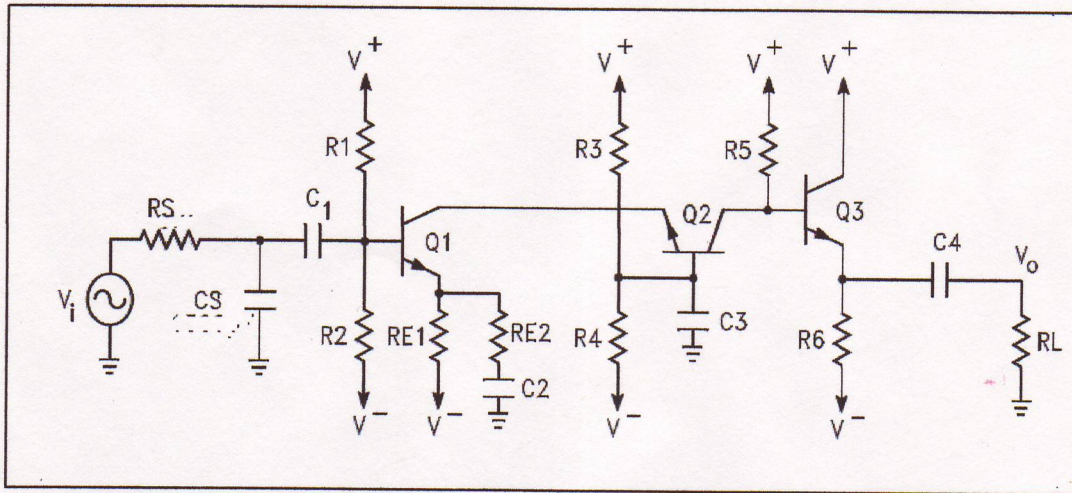


Figure 1: Low-noise amplifier circuit topology used for the design.

### Part 2: Performance and Component Specifications

- DC Rail Power Supplies:  $\pm 15$  V.
- Voltage Gain: 40 dB.
- Maximum Input Signal:  $200 \mu V_{\text{rms}}$ .
- Lower Half-Power Cutoff Frequency:  $\leq 20$  Hz.
- Upper Half-Power Cutoff Frequency:  $\geq 20$  kHz.
- Total Harmonic Distortion (THD):  $\leq 0.4$  % at an output signal level of +10 dBm across a  $600 \Omega$  load resistor (according to standard audio signal level specifications) for an input sine wave with a frequency of 2 kHz. This is equivalent to a  $\sim 2.45 V_{\text{rms}}$  waveform across the load  $R_L$ .
- Source Impedance:  $R_S = 200 \Omega$ .
- Shunt Capacitance at the input:  $C_S = 10$  nF.

- Load Resistance  $R_L = 3 \text{ k}\Omega$ .
- Equivalent input noise voltage over the band 20 Hz to 20 kHz:  $\leq 1 \text{ }\mu\text{V}$
- Active device choice: NPN BJT 2N3904 or 2N4401 measured during an earlier laboratory experiment must be used.
- Power supply decoupling network needs to be used for the rails.

### **Part 3: Simulation Specifications**

The initial proposed design needs to be verified with SPICE circuit simulations. This simulation phase should precede the circuit assembly phase.

The default values for the BJT model parameters (IS, BF, RB, VA, CJC, CJE, TF) provided by the SPICE simulator should not be used. The values obtained from curve tracer measurements and manufacturer's datasheets must be used. The value of base spreading resistance ( $r_x$ ) measured during an earlier experiment should be used as the SPICE model parameter RB.

A noise simulation of the circuit should be made to predict the signal-to-noise ratio (SNR) corresponding to an output signal level of +10 dBm into a load resistance of 600  $\Omega$ , as well as the noise figure of the amplifier.

The SPICE simulations should consist of the following parts:

- .OP (to verify the biasing or quiescent or the DC operating point of the circuit)
- .AC (to verify the frequency response and phase margin specifications)
- .TRAN (to examine the clipping and slew rate performance)
- .FOUR (to verify the THD specification)
- .NOISE (to verify the noise specifications)

### **Part 4: Measurement Specifications**

The following parameters needs to be measured and reported for the designed circuit assembled on a breadboard.

- Mid-band Voltage Gain.
- -3 dB (or half power) bandwidth.
- Positive and Negative slew rates.
- THD at  $f = 2 \text{ kHz}$  according to the conditions specified earlier.
- Quiescent operating point of the circuit.
- Output DC offset with input grounded.
- Equivalent input noise voltage.
- Signal-to-Noise-Ratio (SNR).
- Noise Figure: Spot Noise Figure at  $f = 2 \text{ kHz}$  and the Total Noise Figure.

## Design Philosophy

### Gain and THD considerations

In the following description, transistor names refer to that on Figure 1, while voltages and currents with subscripts ending in 1, 2, and 3 refers to the transistor  $Q_1$ ,  $Q_2$ , and  $Q_3$  respectively.

The front stage of the amplifier is a cascode combination. In this configuration,  $Q_2$  produces almost all of the voltage gain, while  $Q_1$  provides some current gain and a low voltage gain (due to the low input impedance of the common-base stage  $Q_2$ ), which reduces the high-frequency feedback through Miller effect.  $Q_1$  does raise the power level of the input signal to some extent. Given that the output stage ( $Q_3$ ) is a common-collector configuration, it has a voltage gain close to unity. Therefore,  $Q_2$  and its associated  $R_5$  must be designed for voltage gain. Since we desire a very low THD, it is important that  $V_{CE2}$  is kept as large as possible, to allow for operation well within the linear region of  $Q_2$ . The same is true for  $Q_3$ . Note that while simply increasing  $R_5$  is a tempting way to increase the gain, this also reduces  $V_{CE2}$ , which negatively affects the THD. To prevent this, if  $R_5$  must be increased,  $I_{C1}$  must also be reduced. It is also desirable to operate  $Q_2$  at a higher current level for an improved gain-bandwidth product.

$R_{E2}$ , the negative feedback resistor at the emitter of  $Q_1$ , is critical in determining the overall gain of the circuit as well. As the gain of the  $Q_1$  stage is low, it must be kept in mind that any small changes in it will be further multiplied by  $Q_2$ . This suggests that it is relatively easy to change the overall gain by simply tweaking  $R_{E2}$ . However, the gain provided by  $Q_1$  must be kept low because  $V_{CE1}$  is relatively small, and an increased voltage swing can drive  $Q_1$  into a highly non-linear region of operation, which worsens the THD. Therefore, even though no specific theoretical design for THD will be conducted, we will design for the best possible THD by biasing  $Q_2$  and  $Q_3$  in their linear region of operation, and  $Q_1$  with a relatively low voltage gain, i.e., trying to keep  $R_{E2}$  relatively large for a feedback resistor (hundreds of ohms). Thus, keeping in mind THD considerations for the design, the base biasing network for  $Q_2$  is designed so that  $V_{CE2}$  is as large as possible (approximately 10 V). The reason this is possible is because by lowering  $V_{B2}$ , and assuming linear operation of  $Q_2$ ,  $V_{E2}$  is also lowered, which increases  $V_{CE2}$ . The resistor used in this network will be small (tens of kilo-ohms) compared to those that bias  $Q_1$  (few mega-ohms) in order to make  $V_{B2}$  relatively insensitive to changes in  $I_{C2}$ .

Our choice of  $V_{CE2}$  being approximately 10V stems from the fact that  $V_{B3}$  must be approximately between 0V and 5V in order for  $Q_3$  to operate in a linear region. This implies that  $V_{B1}$  is going to be between -10V and -15V (close to the

negative rail). However, we don't want to bias the base of Q1 too close to the negative rail because this calls for a small  $R_2$ , which worsens noise, as explained next.

## Noise considerations

Clearly, the largest noise contribution happens at the input of the front stage. The base biasing network of Q1 (formed by resistors  $R_1$  and  $R_2$ ) effectively presents a shunt resistance to the input of the amplifier. Therefore, it is important to use resistors as large as possible for this network (~ few mega-ohms or hundreds of kilo-ohms). The first step will be to determine the optimum-noise collector current for the cascode combination ( $I_C$  is approximately the same for both Q1 and Q2). Once this current is known, the base biasing network for the first stage is designed.

Another large contribution to the total noise is expected from the cascode combination of Q1 and Q2. One cannot simply state that Q1 is the largest contributor to noise. Since the voltage gain of the Q1 stage is low, the noise contribution of Q2 can be significant too. Therefore, in finding the optimum-noise collector current for Q1 and Q2, we will analyze the cascode combination and not just Q1 alone.

It is important to note that similar noise performance could be obtained with quite different frequency response of the amplifier. The topology used here is similar to using an overall feedback to get low-noise performance while simultaneously optimizing the gain-bandwidth product of the amplifier.

## Device Parameter Measurements

 


Figure 2: Representative output characteristics of a 2N3904 NPN BJT device.

The 2N3904 discrete NPN BJT device was chosen to be used for the low-noise amplifier design. Noise measurements were earlier performed on this device as a part of Lab 4 along with 2N4401, but the measurement results did not show much difference in noise performance between the two transistors. Most other parameters of interest are very close for these two transistors. 2N3904 was finally chosen as the device of interest for this design.

 


Figure 3: Representative  $I_C$  vs  $V_{BE}$  plot of a 2N3904 BJT NPN device.

Output characteristics of the 2N3904 devices (as in Figure 2) were used to calculate  $\beta$ ,  $V_A$ ,  $R_o$  for the transistors. From the previous laboratory experiment, the measured value of  $r_x$  was used. The rest of the relevant BJT SPICE model parameters were extracted from the manufacturer's datasheet. This modified BJT SPICE device model was used for the circuit simulations performed in the next part of the design procedure. This helps to make the models more realistic, which when used for designing circuits, would potentially give more reliable circuit simulation results.

## Theoretical Calculations

### Optimum-noise collector current for $Q_1$ and $Q_2$

A theoretical derivation for the optimum-noise collector current for the cascode combination was performed from equation 7.119 in the class notes, when flicker noise is neglected and it is assumed that  $I_{C1} \approx I_{C2}$ . Only the result is shown here:

$$I_{C(OPT)}^2 = \frac{\alpha\beta^2(\alpha\beta + 1)V_T^2}{\alpha\beta^2(R_1 + r_{x1} + R_2)^2 + \alpha\beta[R_1 + r_{x1} + (\beta + 1)R_2]} \quad (1)$$

Where,

$\beta = \beta_1 = \beta_2$	:	common-emitter current gain for $Q_1$ and $Q_2$ (assumed equal)
$\alpha = \alpha_1 = \alpha_2$	:	common-base current gain for $Q_1$ and $Q_2$ (assumed equal)
$r_{x1}$	:	base spreading resistance of $Q_1$
$R_1$	:	(AC) source equivalent resistance
$R_2$	:	(AC) $Q_1$ external emitter equivalent resistance

For  $\beta = 320$ ,  $r_{x1} = 30 \Omega$ ,  $R_1 = 200 \Omega$ ,  $R_2 = 400 \Omega$ , the collector current that gives the optimum noise for the configuration is found to be  $I_{C(OPT)} = 710 \mu A$ .

While Equation 1 above gives a good starting point for  $I_C$ , the fact that flicker noise was neglected will be found to be a weak assumption. A lower  $I_C$  will be used in an attempt to reduce flicker noise (which is directly proportional to  $I_C$ ), and thus the total noise band power.

### Small-signal voltage gain

A theoretical derivation for the overall small-signal voltage gain has been performed as well. In this derivation, the  $r_{out}$  (output impedance) of the BJTs was considered to be very large and thus neglected (based on measurements performed earlier during lab experiments). Also, the  $\beta$  (current-gain) for the transistors were considered to be large. Only the result is presented here:

$$A_v \approx \beta_1 \beta_3 \frac{R_5}{R_5 + r_{\pi 3} + (\beta + 1)r_{out}} \cdot \frac{r_{out}}{R_S + r_{\pi 1} + (\beta_1 + 1)r_{e,1}} \approx \left[ \frac{R_5}{r_{e,1} + \frac{R_S + r_{\pi 1}}{\beta_1}} \right] \left[ \frac{r_{out}}{r_{out} + \frac{R_5 + r_{\pi 3}}{\beta_3}} \right] \quad (2)$$

Where,

$r_{out}$	:	$R_6 // R_L$ , the equivalent load resistance at the output
$r_{e,1}$	:	$R_{E1} // R_{E2}$

As expected,  $R_5$  and  $r_{e,1}$  (the equivalent emitter AC resistance of  $Q_1$ ) play an important role in determining the gain. The design procedure will first fix  $r_{out}$  based on  $Q_3$  biasing considerations, which will then leave  $R_5$  and  $R_{E2}$  as the most important contributors to the voltage gain. A constant ratio between  $R_5$  and  $R_{E1}$  will keep the bias voltages approximately constant for  $Q_1$  and  $Q_2$ .

### Theoretical calculations for component values

A first set of values for the passive components based on the following rationale were computed and is shown below:

- All capacitors large enough to obtain a low lower cut-off frequency: **47  $\mu F$** .
- $\beta = 320$  for all BJTs.
- For low noise:  $I_{C1} = I_{C(OPT)} = 710 \mu A$ . Thus,  $I_{B1} = 2.21 \mu A$ .

- For large voltage swing at the output:  $I_{C3} = 2 \text{ mA}$ ,  $V_{E3} = 0 \text{ V}$ . Thus,  **$R_6 = 7.5 \text{ k}\Omega$** .
- $r_{out} = R_6 // R_L = 2.14 \text{ k}\Omega$ .
- $r_{\pi 1} = \beta_1 V_T / I_{C1} = 11.3 \text{ k}\Omega$ .
- $r_{\pi 3} = \beta_3 V_T / I_{C3} = 4.0 \text{ k}\Omega$ .
- Choose  $R_1$  as a very large resistor:  **$R_1 = 3 \text{ M}\Omega$** .
- Select  $V_{B1}$  to be between  $-10 \text{ V}$  and  $-15 \text{ V}$ , not too close to  $-15 \text{ V}$ :  $V_{B1} = -11 \text{ V}$ .
- Thus,  $R_2$  can be computed:  **$R_2 = 620 \text{ k}\Omega$** .
- **$R_{E1} = (V_{B1} - V_{BE1}) / I_{E1} = 4.7 \text{ k}\Omega$** .
- Total current through  $R_5$ :  $I_{R5} = I_{C(OPT)} + (I_{C3} / \beta_3) = 716 \mu\text{A}$ .
- Therefore,  **$R_5 = (+15 \text{ V} - 0.7 \text{ V}) / I_{R5} = 20 \text{ k}\Omega$** .
- To achieve  $A_v = 100$ , from equation 2,  $r_{e1} = 157 \Omega$ . Thus,  **$R_{E2} = 162 \Omega$** .
- $R_3$  and  $R_4$  are chosen somewhat arbitrarily to ensure that  $V_{B2} = -5 \text{ V}$ . Make the sum of its resistances no more than  $40 \text{ k}\Omega$  (see the THD considerations section). Thus,  **$R_3 = 27 \text{ k}\Omega$**  and  **$R_4 = 13 \text{ k}\Omega$** .

The next phase in the design procedure is to simulate the circuit with the component values calculated theoretically above.



## Circuit Simulation Results

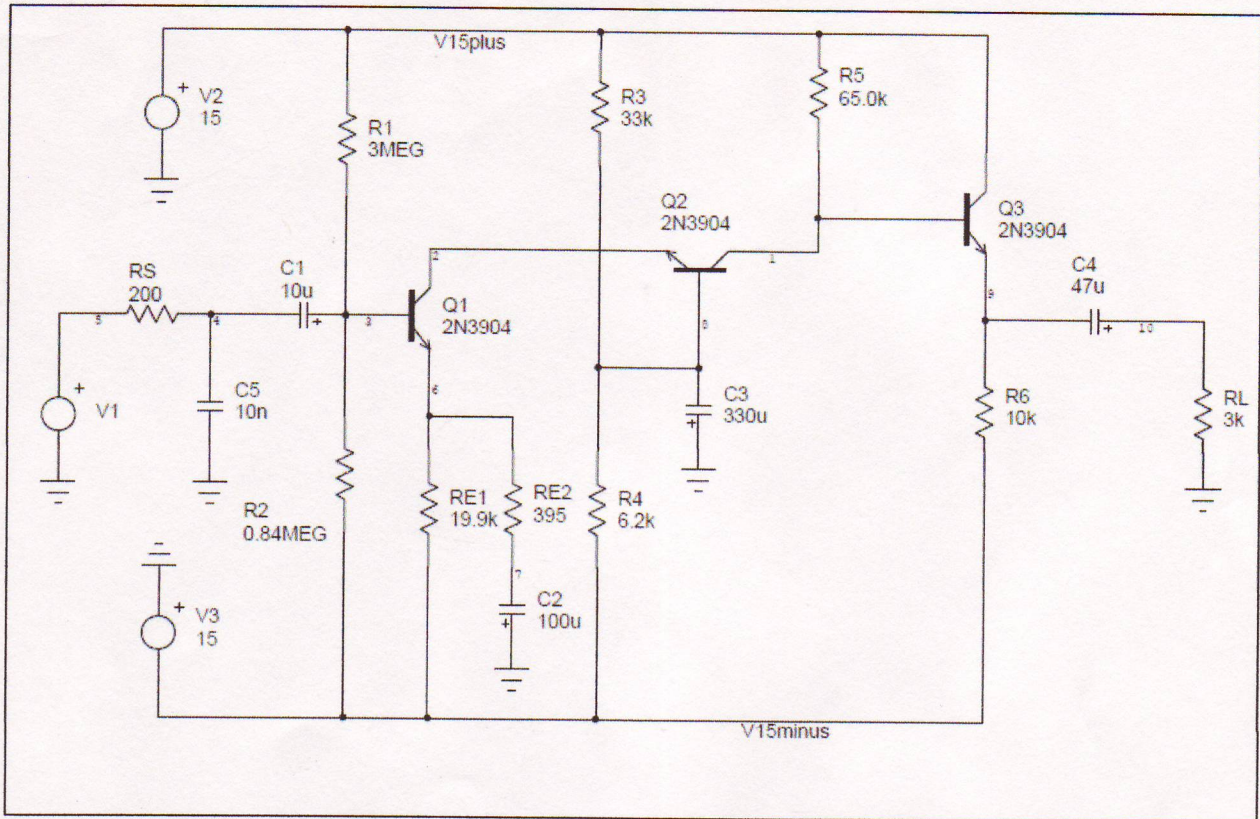


Figure 4: Circuit used for simulations.

- Multiple SPICE based circuit simulation software packages were tried like LTSpice, Agilent ADS, etc. Finally, Intusoft SPICE was used as the circuit simulation software of choice to optimize convenience with access, installation and capabilities of the package.
- A snapshot of the circuit schematic used for the simulations is shown in Figure 4.
- The following simulation deck shows the BJT model used:

```
.AC DEC 1001 1 1MEG
.OP
.TRAN 0.005M 5M 0 0.005M
.NOISE V(10) V1 DEC 1001 20 20K 1
.PRINT NOISE INOISE ONOISE
.FOUR 2000 V(10)
.OPTIONS ACCT
Q1 2 3 6 _Q1_MOD
.MODEL _Q1_MOD NPN AF=1.0 BF=320 BR=7.5 CJC=3.5PF CJE=4.5PF
+ IKF=.025 IS=1.4E-14 ISE=3E-13 KF=9E-16 NE=1.5 RB=30 RC=2.4
+ TF=4E-10 TR=21E-9 VAF=231 XTB=1.5
Q2 1 8 2 _Q2_MOD
```

```

.MODEL _Q2_MOD NPN AF=1.0 BF=320 BR=7.5 CJC=3.5PF CJE=4.5PF
+ IKF=.025 IS=1.4E-14 ISE=3E-13 KF=9E-16 NE=1.5 RB=30 RC=2.4
+ TF=4E-10 TR=21E-9 VAF=93.92 XTB=1.5
Q3 V15PLUS 1 9 _Q3_MOD
.MODEL _Q3_MOD NPN AF=1.0 BF=320 BR=7.5 CJC=3.5PF CJE=4.5PF
+ IKF=.025 IS=1.4E-14 ISE=3E-13 KF=9E-16 NE=1.5 RB=30 RC=2.4
+ TF=4E-10 TR=21E-9 VAF=116.72 XTB=1.5
R1 V15PLUS 3 3MEG
R2 3 V15MINUS 0.84MEG
C5 4 0 10N
RS 5 4 200
V1 5 0 DC=0 AC=1 SIN 0 35.4M 2K 0
RE1 6 V15MINUS 19.9K
RE2 6 7 395
R5 V15PLUS 1 65.0K
C2 0 7 100U
R3 V15PLUS 8 33K
R4 8 V15MINUS 6.2K
C3 0 8 330U
R6 9 V15MINUS 10K
C4 10 9 47U
RL 10 0 3K
C1 3 4 10U
V2 V15PLUS 0 DC=15 AC=0
V3 0 V15MINUS DC=15 AC=0
.END

.END

```

## **Circuit Simulation Tradeoffs**

The following tradeoffs were encountered while designing the circuit for the specified performance levels:

- Increasing gain by simply lowering  $R_{E2}$  worsens (increases in percentage) THD.
- Increasing gain with  $R_5$  worsens THD.
- Increasing gain by lowering  $R_{E1}$  changes THD. There was an optimum value for  $R_{E1}$ , around 19.9k $\Omega$ . This is due to a change in the bias point of  $Q_1$  as a result of changing  $R_{E1}$ .
- Simultaneously changing  $R_{E2}$  and  $R_5$  helped in minimizing THD.
- Increasing the current in  $Q_3$  by reducing  $R_6$  helps in minimizing the THD at the output to some extent. Again, there was an optimum value for  $R_6$ .
- Reducing  $V_{B1}$  by reducing  $R_2$  helps in getting a much higher voltage swing at the output but increases the noise if the value is small enough.
- $I_{C1}$  and  $I_{C2}$  can be increased by reducing  $R_5$  and  $R_{E1}$ , but their ratios should be constant to keep  $V_{CE1}$  and  $V_{CE2}$  at a fixed level.
- Tweaking some of the capacitors can change THD, but only to a very small level.

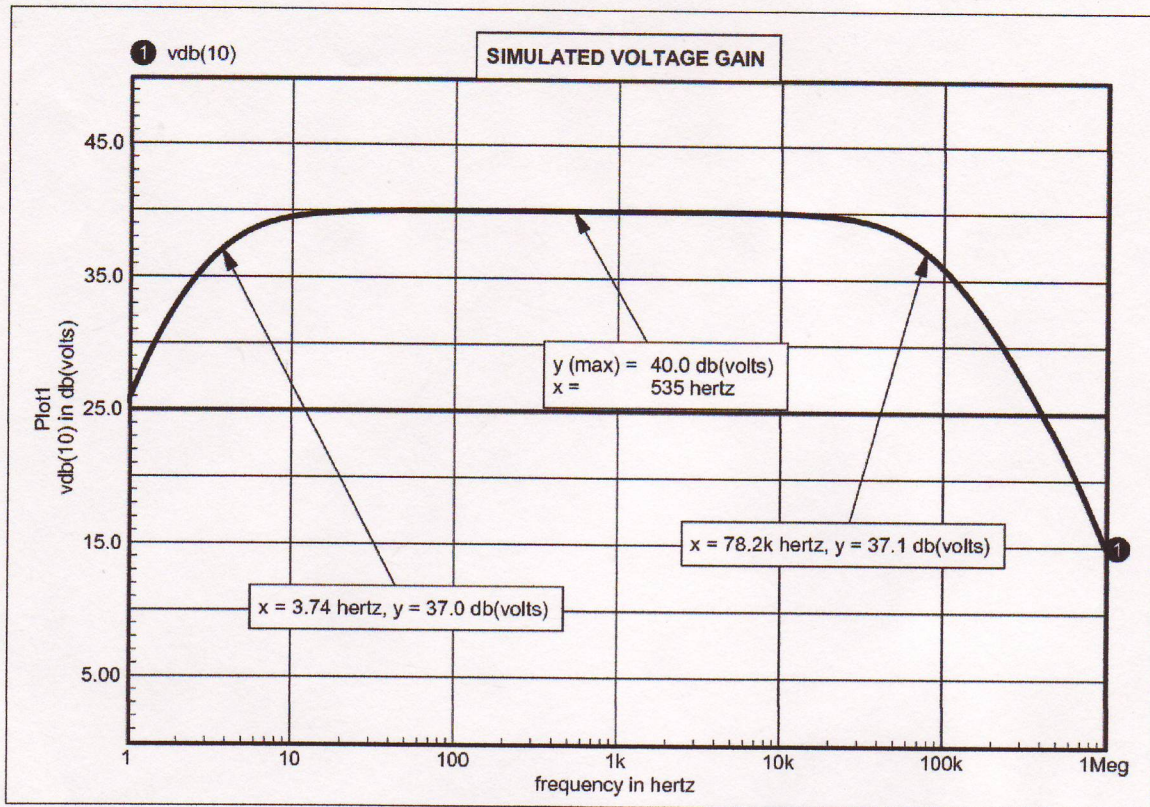


Figure 5: Simulated voltage gain of the circuit.

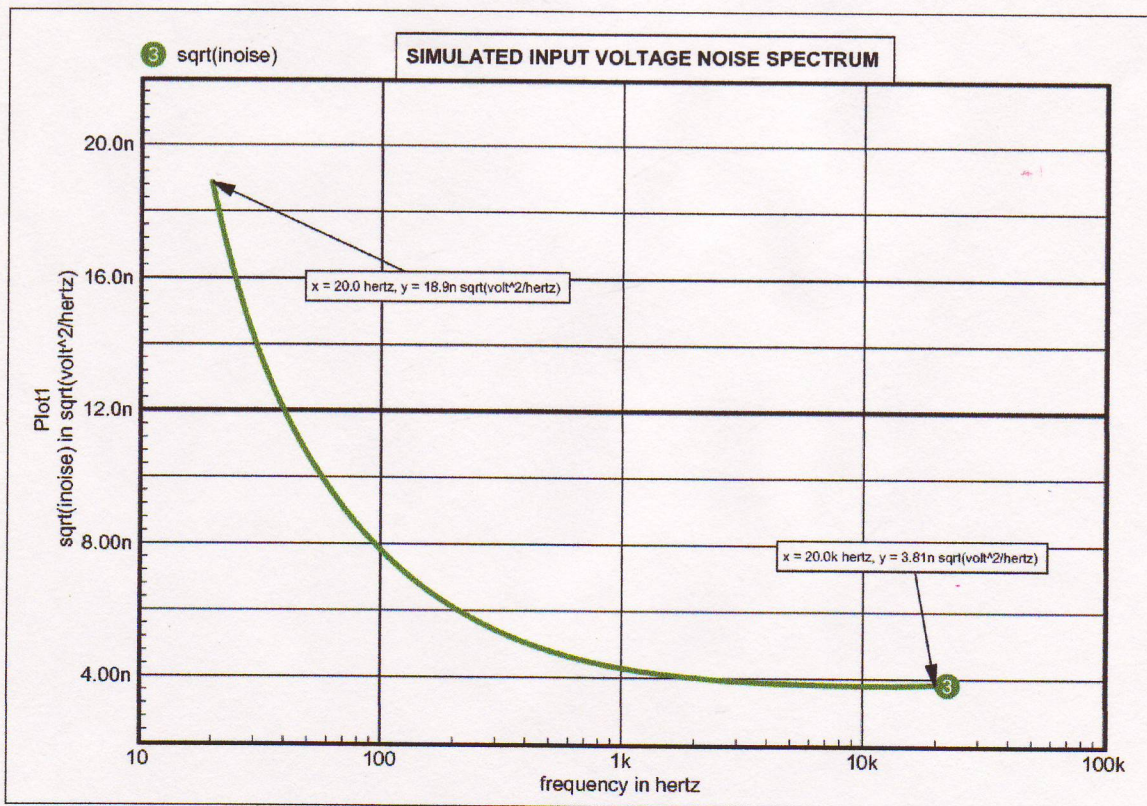


Figure 6: Simulated equivalent input noise spectrum of the circuit.

## Experimental Results

 


Figure 6: Snapshot of the assembled circuit on breadboard. Note that the output stage (right) was placed away from the cascode combination (left) to prevent positive feedback that could lead to oscillations.

### Frequency Response Measurement

- The HP 33120A Function Generator (a  $24.5 \text{ mV}_{\text{rms}}$  sine wave output with 2 kHz frequency and  $50 \Omega$  output resistance) was used for measuring the gain and bandwidth of the amplifier. The output waveforms were measured on the Tektronix 754D Digital Oscilloscope. The frequency of the input signal was varied over a wide range to calculate the gain of the op-amp stage alone. The measured input voltage  $V_i$  at 2 kHz =  $24.59 \text{ mV}_{\text{rms}}$ .
- The measured output voltage  $V_o$  at 2 kHz (mid-band) =  $2.493 \text{ V}_{\text{rms}}$ .
- The -3dB frequencies were measured as  $f_L = 17.8 \text{ Hz}$  and  $f_H = 77 \text{ kHz}$ .
- The -3dB (or half-power) frequencies were identified as frequency points where the output voltage was  $1/\sqrt{2}$  times the mid-band output voltage. For this the frequency was varied continuously using the function generator.
- The measured gain = 101, which is  $> 40 \text{ dB}$  and satisfy the design specification for the amplifier.

### Total Harmonic Distortion Measurement

In order to measure THD, a 2 kHz sinusoidal input signal is fed to the amplifier such that the output is a waveform with  $2.45 \text{ V}_{\text{rms}}$  (+10 dBm for a 600 ohm resistor audio standard). The THD of this output signal is then measured with the DSA. The input and the output signal during the THD measurement

are shown in Figures 7 and 8. The spectrum of the output signal including the fundamental and harmonic frequencies is shown in Figure 9.

 


Figure 7: Output waveform at +10 dBm for THD measurements and voltage gain calculations.

 


Figure 8: Input waveform corresponding to +10 dBm output for voltage gain calculations.

Marker Fcn Trace: A  
[Harmonic]

Fund: 2 kHz  
Num Harms: 12

Date: 12-06-08 Time: 01:27:00 AM

RMT SR

A 12 C 12

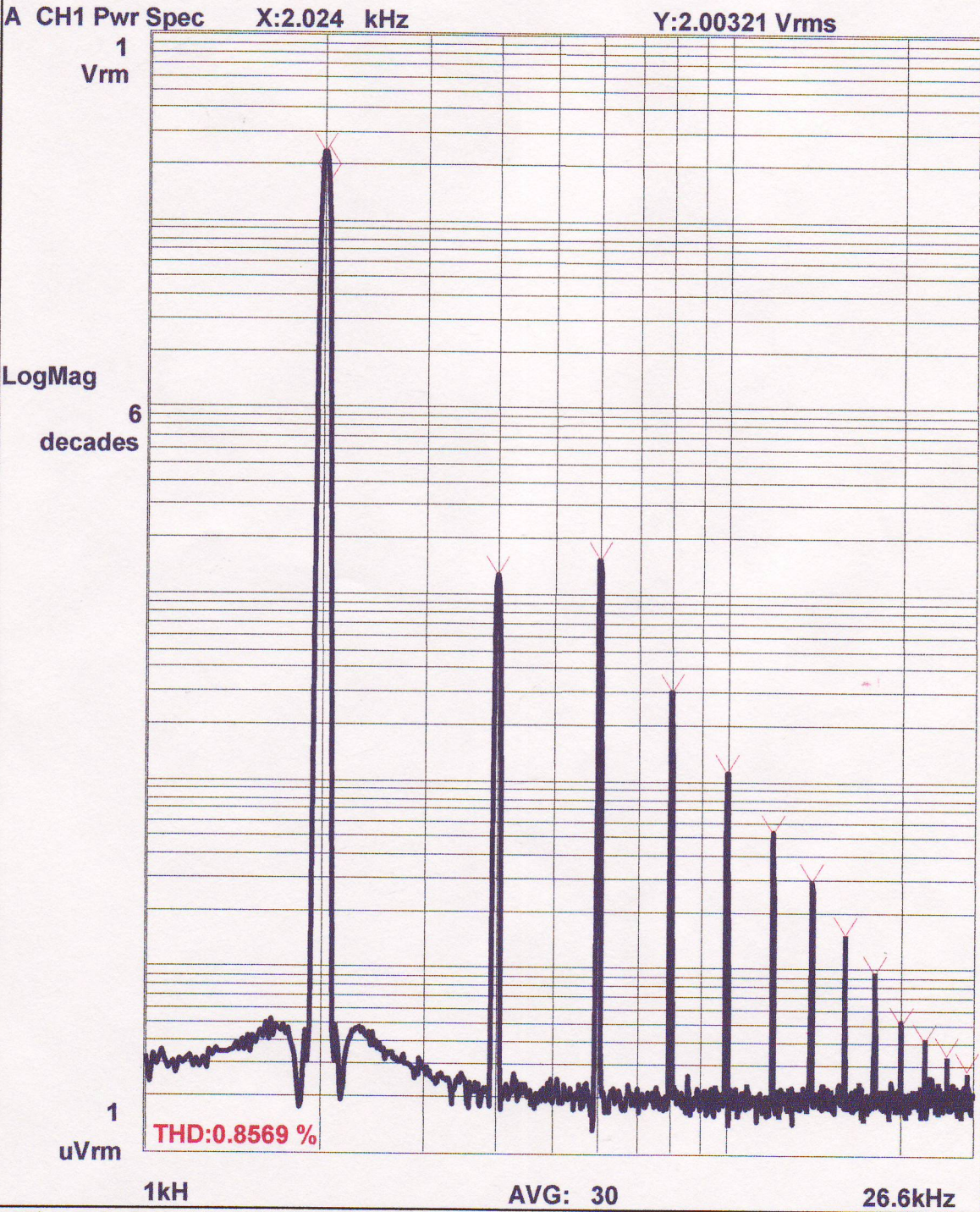


Figure 9: Spectrum of the output waveform of the amplifier from THD measurement.

A high peak for the third-harmonic in Figure 9 indicates that the output voltage swing is asymmetric, which was proved right as the negative swing was clipped before the positive swing when the output signal level was increased (beyond specifications, just for verification purposes).

## **Noise Measurement**

The component values used for the simulation deck led to a much higher noise level experimentally than predicted by simulation results. The reason was attributed to a high flicker noise component at the theoretical optimum  $I_C$  for  $Q_1$  and  $Q_2$ . This led to the decision of using a lower than optimum  $I_C$  for biasing  $Q_1$  and  $Q_2$ . It was experimentally determined that  $I_C \sim 200 \mu\text{A}$  brought the total input noise down, and therefore, this collector current level was chosen. Additionally, in order to lower flicker noise further down, the lower cut-off frequency was raised from 3 Hz to 17 Hz. This was achieved by reducing  $C_1$  from 47  $\mu\text{F}$  to 1  $\mu\text{F}$ . The total and spot noise were measured when the input was shorted ( $R_S = 200 \Omega$ ). The SNR and noise figure were computed as follows:

$$SNR = 10 \log \left( \frac{v_{so}^2}{v_{no}^2} \right)$$

$$NF = 10 \log \left( \frac{\frac{v_{ni}^2}{\Delta f}}{4kT_o R_S} \right) \quad (3)$$

Where,

$v_{so}$  : amplitude of the output waveform  
 $v_{no}$  : total output noise voltage  
 $v_{ni}$  : total input noise voltage

All of these helped in reducing the equivalent output noise voltage, which was measured using the DSA. The final measured equivalent output noise voltage is shown in Figure 10 below. When this value is divided by the voltage gain  $A_v$ , it gives the equivalent input noise voltage. From the measured value in Figure 10, the equivalent input noise voltage is  $< 1 \mu\text{V}$ , which satisfies the target design specification for the amplifier. The bandwidth used for measurement of the spot noise voltage by the DSA is 61.11 Hz.

The SNR, the Noise Figure at 2 kHz and the Total Noise Figure for the amplifier are calculated using the measurement data in Figure 10 (total band 20Hz to 20kHz noise RMS-voltage, or  $v_{no}$ ) and are provided in Table 1 below. All noise measurements were done when the input was grounded. To get a pessimistic noise measurement, we substituted the function generator with a 50 $\Omega$  resistor to ground, in addition to the 150 $\Omega$  resistor already in place.

 


Figure 10: Noise Spectrum measured at the output of the amplifier.



## Slew-Rate Measurement

Slew rate measurements were performed by feeding the amplifier with a 25 mV<sub>rms</sub> square wave at 2 kHz frequency (high enough to see the slope in the output waveform corresponding to the edges of the input square waveform). The maximum slope of the rising and falling edges of the output waveform were measured and recorded as positive and negative slew rates respectively. Figures 11 and 12 show the rising and falling edges of the output waveform respectively along with the slew rate measurement setup. The positive and negative slew rates measured were 1.44 V/ $\mu$ s and 1.4 V/ $\mu$ s respectively.

 


Figure 11: Positive slew rate measurement.

 


Figure 12: Negative slew rate measurement.

## **Experimental Tradeoffs**

Most of the tradeoffs encountered while assembling and testing the designed circuit on a breadboard includes the issues which were assessed theoretically and/or by simulations and has been discussed earlier in this report.

The various tradeoffs taken care of during the noise measurements were the most dominant ones. In each case, either or both gain and THD were the tradeoffs to minimize noise. In an extreme case, changing capacitors to affect the noise and THD could adversely affect the frequency response of the amplifier.

Deviations of the experimental design and results from the simulated version could be attributed to the deviation of actual device parameter values from those used in simulations. Temperature should also be kept in mind, as the lab where the measurements were taken was, at times, considerably warmer than  $T_0$ ). We found that the DC circuit performance was very sensitive to the (ratio) of values of  $R_1$  and  $R_2$ , as these components play a big role in fixing  $V_{B1}$ . The circuit AC performance is sensitive to some of the component values (in particular  $R_5$  and  $R_{E2}$ ), and since the component values are different from their nominal values due to tolerance in their values, some of these experimental variations (compared to simulation) can be attributed to the distribution of component values.

Table 1: Simulated and realized circuit performance and components.

Parameter	Simulated	Realized or measured (nominal) <i>(final values, after circuit modifications)</i>
$A_v$ (Voltage Gain)	40.0 dB	40.1 dB
$f_L$ (lower -3dB frequency)	3.74 Hz	17.8 Hz
$f_H$ (upper -3dB frequency)	74.2 kHz	77.0 kHz
Output Offset Voltage	0 V	50 $\mu$ V
Max. output voltage swing	7.25 $V_{pp}$	7 $V_{pp}$
Max. input voltage swing	74.9 mV $_{pp}$	71.1 mV $_{pp}$
THD	0.95 %	0.86 %
$v_{ni}$	0.558 $\mu$ V $_{rms}$	0.988 $\mu$ V $_{rms}$
Positive Slew Rate	1.52 V/ $\mu$ s	1.44 V/ $\mu$ s
Negative Slew Rate	1.50 V/ $\mu$ s	1.40 V/ $\mu$ s
SNR	92.5 dB	87.8 dB
NF @ 2 kHz	6.99 dB	8.44 dB
Total NF	6.86 dB	11.8 dB
$V_{B1}$	-10.4 V	-10.46 V
$V_{CE1}$	0.10 V	0.15 V
$V_{CE2}$	12.34 V	11.34 V
$V_{CE3}$	14.22	14.64 V
$I_{C1}$	202 $\mu$ A	200 $\mu$ A
$I_{C2}$	204 $\mu$ A	205 $\mu$ A
$I_{C3}$	1.58 mA	1.57 mA
$R_1$	3.0 M $\Omega$	3.007 M $\Omega$ (3 M $\Omega$ )
$R_2$	0.84 M $\Omega$	894.1 k $\Omega$ (880 k $\Omega$ )*
$R_{E1}$	19.9 k $\Omega$	19.73 k $\Omega$ (20 k $\Omega$ )
$R_{E2}$	395.0 k $\Omega$	389.1 $\Omega$ (390 $\Omega$ )
$R_3$	33.0 k $\Omega$	32.77 k $\Omega$ (33 k $\Omega$ )
$R_4$	6.2 k $\Omega$	6.11 k $\Omega$ (6.2 k $\Omega$ )
$R_5$	65.0 k $\Omega$	67.58 k $\Omega$ (68.33 k $\Omega$ )*
$R_6$	10.0 k $\Omega$	9.79 k $\Omega$ (10 k $\Omega$ )
$R_L$	3.0 k $\Omega$	2.956 k $\Omega$ (3 k $\Omega$ )
$C_1$	10 $\mu$ F	1 $\mu$ F
$C_2$	100 $\mu$ F	47 $\mu$ F
$C_3$	330 $\mu$ F	47 $\mu$ F
$C_4$	47 $\mu$ F	47 $\mu$ F

\*Notes:

- $R_2$  achieved as a series combination of 750k $\Omega$  and 130k $\Omega$ .
- $R_5$  achieved as a series combination of 68k $\Omega$ , 200 $\Omega$  and 130 $\Omega$ .

## Discussion of Results

The experimental and simulation results are tabulated in Table 1 above for comparison. The following comments can be made about the results:

- The simulation results and experimental results compare very well for the DC bias currents and voltages for the devices.
- The passive component values used for design of the circuit compares closely between simulation and experiment.
- The gain and frequency response of the circuit compares very well between simulation and experiment.
- The experimentally measured noise value is much higher compared to that from simulations, as the setup is not designed to avoid any external interference from other stray noise sources, nor temperature higher than  $T_o$ .
- The measured equivalent input noise voltage meets the specification given for the circuit.
- The measured THD is low, but it does not meet the design specification. This is mainly because of  $Q_1$  which might have been pushed to the edge of the linear region while tweaking around with experimental component values. It was decided to meet the gain, frequency response, and -most importantly- noise specifications while still achieving a THD <1% for the amplifier. ✓
- The THD can be improved to the specified level by reducing  $R_5$ , but gain would be traded-off during the process, even after compensating with  $R_{E2}$ .

## Conclusions

All the design specifications for the low-noise amplifier were met by the design except the THD specification. The main reason for this was because of the input stage moving close to the edge of the linear region almost into saturation. This circuit could be further optimized to reduce the THD and meet all the specifications with further time and effort. Still, THD=0.86% was better than the 0.95% predicted by SPICE, due to minor adjustments to the bias point of  $Q_1$  that were done "in the field".

The measurement technique could be improved by using a much larger breadboard to minimize the noise from capacitive coupling. Additionally, it would definitely help to use a shielded metallic box for the noise measurements. Further improvements could result from using better SPICE device models for circuit simulation of the low-noise amplifier.

It was also verified in this circuit that the theoretical optimum collector current obtained when flicker noise is neglected is not accurate. If low frequencies of operation are of interest -as is the case here- then the collector

current for the front cascade stage should be chosen as small as possible. Another flicker noise-reduction technique that gave good results was to raise the lower cut-off frequency of the amplifier, so that more lower-frequency flicker noise gets "cut-off". One must keep in mind that at the frequencies of tens of Hz, the flicker noise is by far the larger contributor to the total noise.