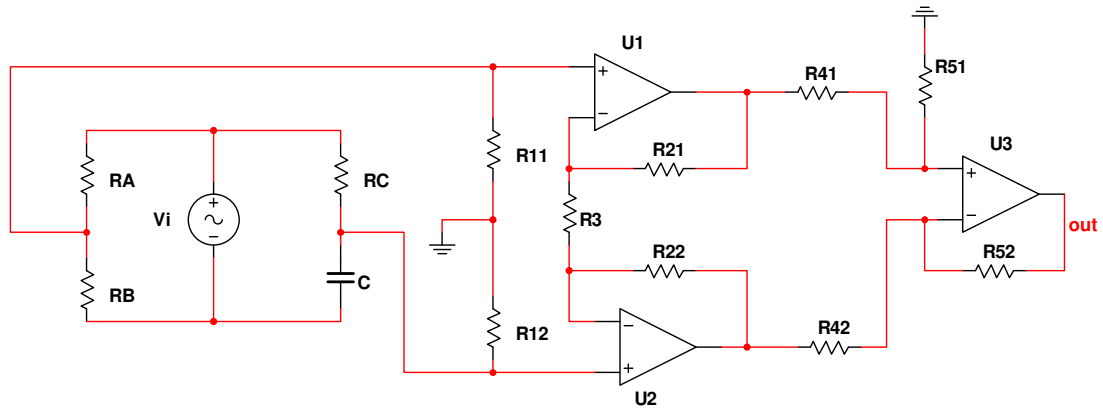


# ECE 3042

## Homework Assignment No. 4

Spring 2013 Homework for Experiment No. 4

Due Week of February 11



1. Shown above is a first order all pass filter. Design the filter so that the phase shift is  $90^\circ$  when  $f = 7.3 \text{ kHz}$  and magnitude of the ratio of the output voltage to the input voltage is 30 for all frequencies when  $v_i$  is a sine wave. Pick the differential input impedance of the instrumentation amplifier to be  $660 \text{ k}\Omega$ .

Use National Instruments SPICE to plot the magnitude and phase of  $T(s) = V_o/V_i$  as the frequency varies from  $100 \text{ Hz}$  to  $100 \text{ kHz}$ .

2. Use National Instruments SPICE to plot the output versus time when the input is a square wave with a dc level of 0, a peak-to-peak value of  $2 \text{ V}$ , and a frequency of  $1 \text{ kHz}$ . Make the plot for two cycles of the input.