

# Georgia Institute of Technology

## School of Electrical and Computer Engineering

ECE 3043

Electrical and Electronic Circuits Laboratory

Verification Sheet

---

---

NAME: \_\_\_\_\_

SECTION: \_\_\_\_\_

AD LOGIN: \_\_\_\_\_

### Experiment 12: BJT CE Amplifier

Procedure	Time Completed	Date Completed	Verification (Must demonstrate circuit)	Points Possible	Points Received
3. Bias				25	
4,5. Small Signal Gain and Freq Response				25	
6. Clipping				25	
<b>7. Spectral Analysis</b>				25	

To be permitted to complete the experiment during the open lab hours, you must complete at least **four** procedures during your scheduled lab period or spend your entire scheduled lab session attempting to do so. A signature below by your lab instructor, Dr. Brewer, or Dr. Robinson permits you to attend the open lab hours to complete the experiment and receive full credit on the report. Without this signature, you may use the open lab to perform the experiment at a 50% penalty.

SIGNATURE: \_\_\_\_\_

DATE: \_\_\_\_\_

## ECE 3043 Check-off Requirements for Experiment 12

Make sure you have made all required measurements before requesting a check-off. For all check-offs, you must demonstrate the circuit or measurement to a lab instructor. All screen captures must have a time/date stamp.

### 4. Bias

- ✓ Collector, base, and emitter voltages and collector current recorded.

### 5, 6 . Gain and Frequency Response

- ✓ Oscilloscope screen capture showing input and output signals and  $V_{pp}$  measurements for each signal.
- ✓ Calculation of the gain.
- ✓ Plot of gain versus frequency made with HPVVE, LabView, or by hand with -3dB frequencies and midband gain labeled and their values recorded.

### 7. Clipping

- ✓ Screen capture showing soft clipping on output and measured positive and negative peak amplitudes (can use max and min functions on scope).
- ✓ Screen capture showing hard clipping on output and measured positive and negative clipping levels (can use max and min functions on scope).
- ✓ Screen capture of XY plot when amplifier is clipped.
- ✓ Calculation of slope of XY plot (use scope cursors).

### 8. Spectral Analysis

- ✓ Screen capture showing fundamental and distortion components of output signal. Increase input if necessary to generate distortion components. The output should not be clipped.
- ✓ Screen capture after adjusting pot to maximize amplitude of fundamental but eliminate distortion components.
- ✓ Screen capture of input and output sine waves after pot adjustment.
- ✓ Measured circuit gain after pot adjustment.
- ✓ Measured pot value (disconnect pot from circuit before measuring).

COMMON EMITTER AMPLIFIER LTSPICE EXAMPLE

VI 1 0 AC 1 SIN(0 0.7 1K)

\*VOLTAGE SOURCE FOR EITHER AC OR TRAN ANALYSIS, ARGUMENTS OF SINE DC LEVEL, AMPLITUDE, FREQ

RB1 2 0 27K

RB2 6 2 150K

RE1 4 0 2K

RE2 4 7 100

RC 6 3 10K

RL 5 0 20K

C1 1 2 0.22U

C2 3 5 10U

CE 7 0 100U

Q 3 2 4 QKITTYCAT

VPLUS 6 0 DC 15

.MODEL QKITTYCAT NPN(IS=10F BF=200 VA=170 CJC=3.6P TF=0.3N RB=10)

\*IS SATURATION CURRENT, BF FORWARD BETA, VA EARLY VOLTAGE,

\*CJC COLLECTION JUNCTION CAPACITANCE, TF FORWARD TRANSIT TIME,

\*RB BASE SPREADING RESISTANCE

\*DO ONE ANALYSIS AT A TIME. PUT AN ASTERISK IN FRONT OF THE OTHERS

\*.OP

\*OP PROVIDES THE Q POINT

.AC DEC 300 10 100MEG

\*.TRAN 0 3M

\*.FOUR 1K V(5)

\*FOURIER ANALYSIS OF VOLTAGE AT NODE 5 WITH 1K AS FUNDAMENTAL FREQUENCY

.PROBE

.END





