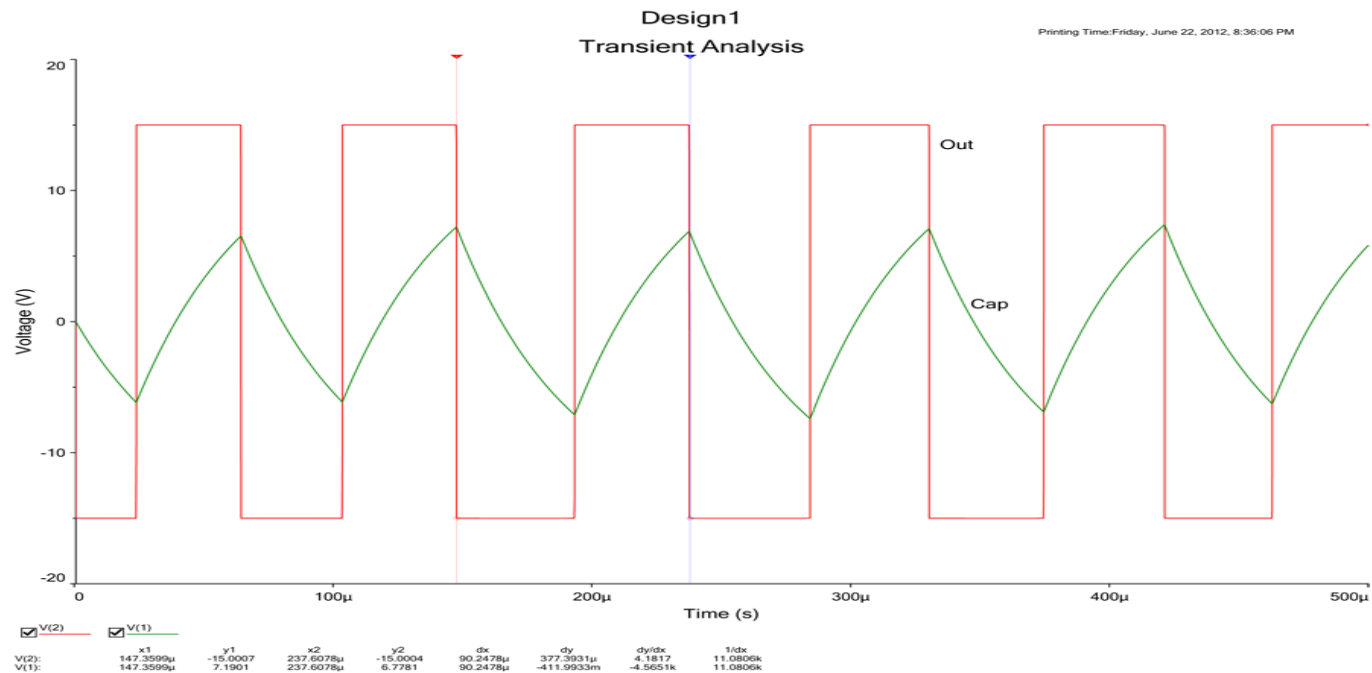



# Single Op Amp

# Relaxation Oscillator



Thomas E. Brewer  
Academic Factotum




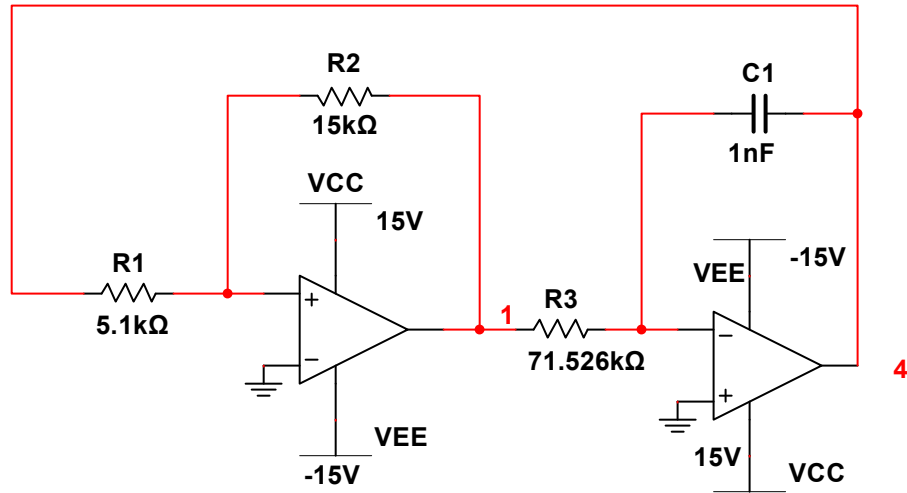

Thomas E. Brewer  
Academic Factotum


Schmitt Trigger Comparator

Integrator

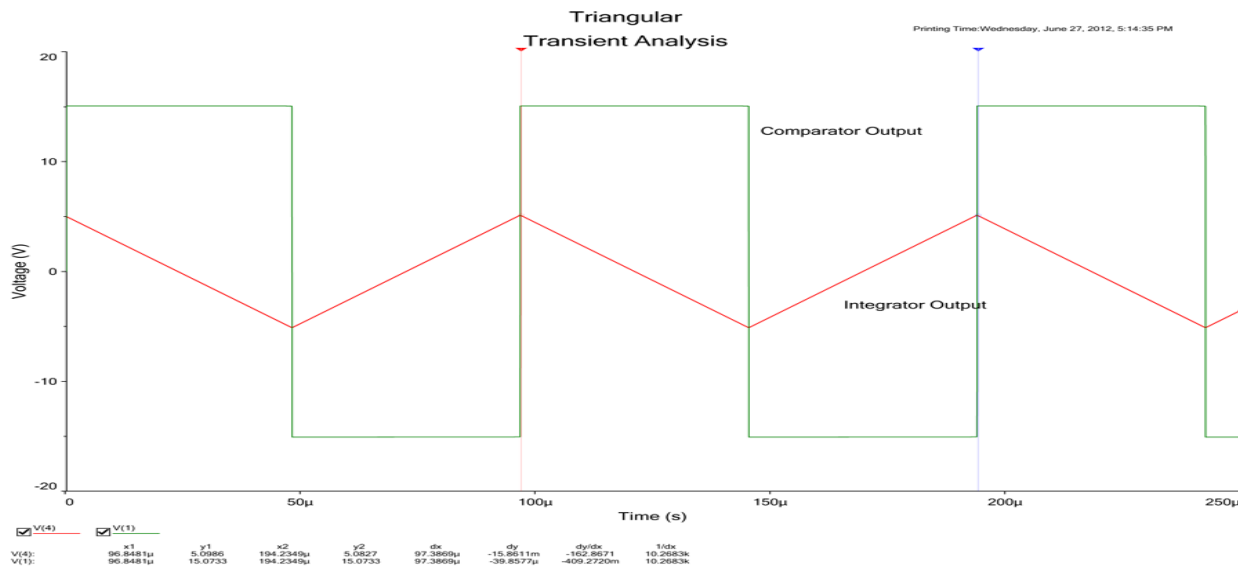


A  
B  
C  
D  
E  
F  
G


A  
B  
C  
D  
E  
F  
G

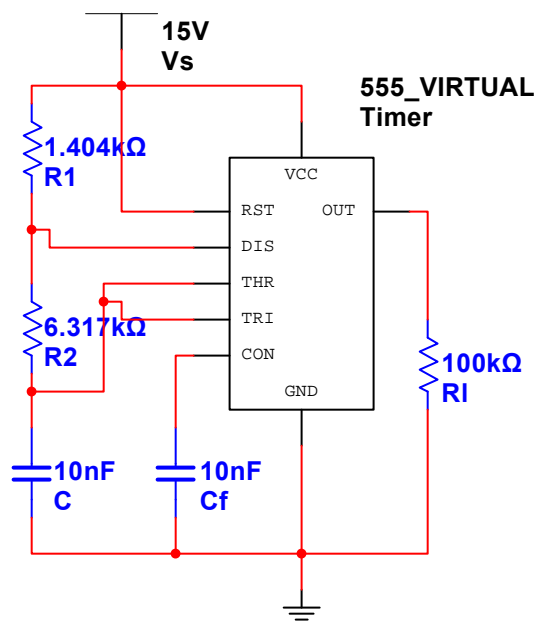

Thomas E. Brewer  
Academic Factotum

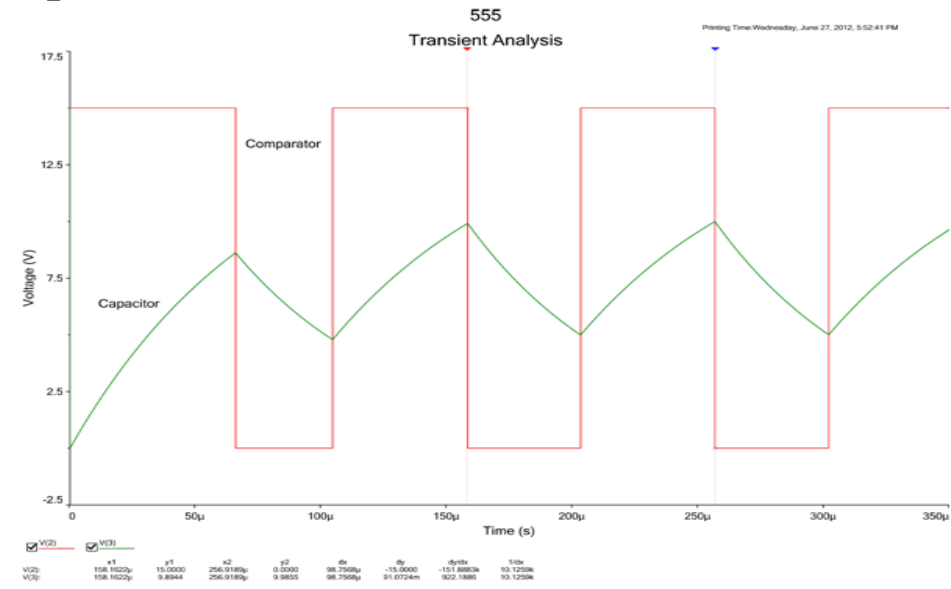


V(6)

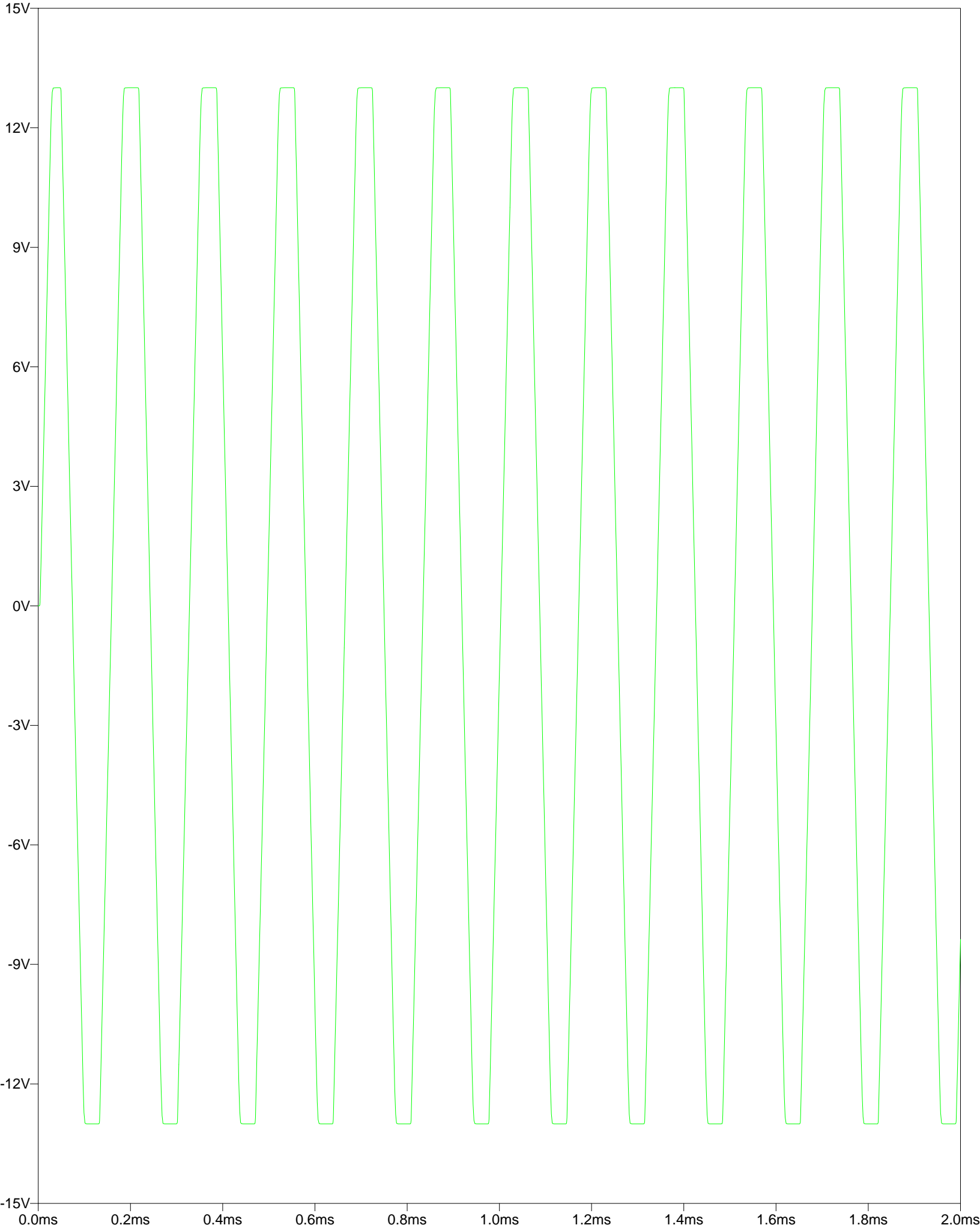

--- Z:\Z\_Red\_Ruby\brewdoc\lece3043hwk\hwk09\_Rel\_Osc\OscCkts\single\_opamp\_741.cir ---

```
Single OpAmp Oscillator
C 2 0 1n IC=0
R 2 6 44.27k
R1 6 3 1k
R2 3 0 1k
X0A 3 2 7 4 6 XUA741
VCC 7 0 DC 15
VEE 4 0 DC -15
*Sngl GenPurpose OpAmp pkgIP8 3,2,7,4,6
..SUBCKT XUA741 1 2 3 4 5
C1 11 12 4.664E-12
C2 6 7 20E-12
DC 5 53 DX
DE 54 5 DX
DLP 90 91 DX
DLN 92 90 DX
DP 4 3 DX
BGND 99 0 V=V(3)*.5 + V(4)*.5
BB 7 99 I=I(VB)*10.61E6 - I(VC)*10E6 + I(VE)*10E6 +
+ I(VLP)*10E6 - I(VLN)*10E6
GA 6 0 11 12 137.7E-6
GCM 0 6 10 99 2.574E-9
IEE 10 4 DC 10.16E-6
HLIM 90 0 VLIM 1K
Q1 11 2 13 QX
Q2 12 1 14 QX
R2 6 9 100E3
RC1 3 11 7.957E3
RC2 3 12 7.957E3
RE1 13 10 2.74E3
RE2 14 10 2.74E3
REE 10 99 19.69E6
RO1 8 5 150
RO2 7 99 150
RP 3 4 18.11E3
VB 9 0 DC 0
VC 3 53 DC 2.6
VE 54 4 DC 2.6
VLIM 7 8 DC 0
VLP 91 0 DC 25
VLN 0 92 DC 25
..MODEL DX D(IS=800E-18)
..MODEL QX NPN(IS=800E-18 BF=62.5)
..ENDS XUA741
.TRAN 0 2m UIC
.PROBE
.END
```

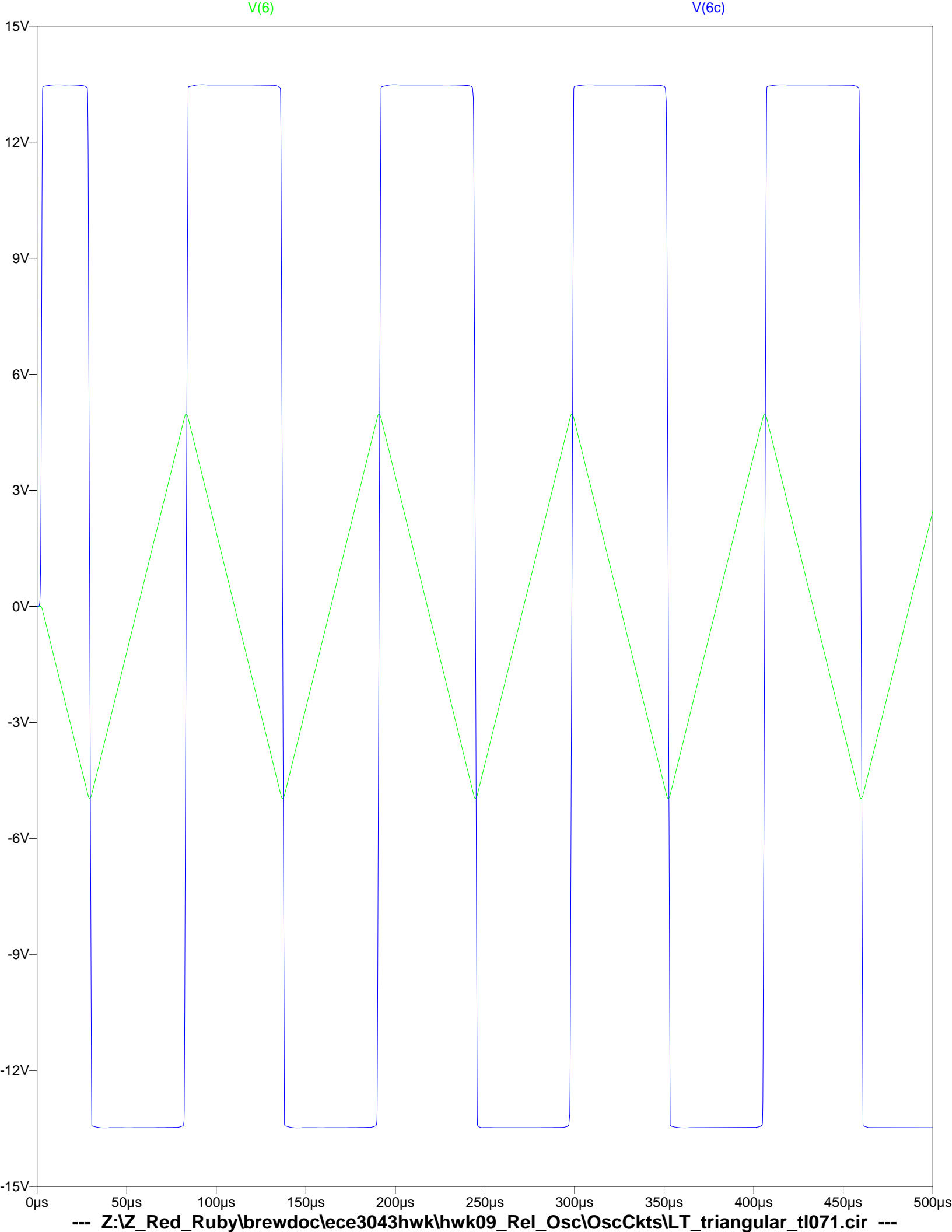

V(6)

V(6c)

--- Z:\Z\_Red\_Ruby\brewdoc\ece3043hwk\hwk09\_Rel\_Osc\OscCkts\LT\_triangular\_t1071.cir ---

```
Triangular Oscillator
C 2 6 1n IC=0
R 6c 2 71.526k
R1 6 3c 5.1k
R2 3c 6c 15k
Xint 0 2 7 4 6 TL071
Xcomp 3c 0 7 4 6c TL071
VCC 7 0 DC 15
VEE 4 0 DC -15
* TL071 OPERATIONAL AMPLIFIER "MACROMODEL" SUBCIRCUIT
* CREATED USING PARTS RELEASE 4.01 ON 06/16/89 AT 13:08
* (REV N/A) SUPPLY VOLTAGE: +/-15V
* CONNECTIONS: NON-INVERTING INPUT
*           | INVERTING INPUT
*           || POSITIVE POWER SUPPLY
*           ||| NEGATIVE POWER SUPPLY
*           |||| OUTPUT
*           |||||
.SUBCKT TL071 1 2 3 4 5
*
C1 11 12 3.498E-12
C2 6 7 15.00E-12
DC 5 53 DX
DE 54 5 DX
DLP 90 91 DX
DLN 92 90 DX
DP 4 3 DX
EGND 99 0 POLY(2) (3,0) (4,0) 0 .5 .5
FB 7 99 POLY(5) VB VC VE VLP VLN 0 4.715E6 -5E6 5E6 5E6 -5E6
GA 6 0 11 12 282.8E-6
GCM 0 6 10 99 8.942E-9
ISS 3 10 DC 195.0E-6
HLIM 90 0 VLIM 1K
J1 11 2 10 JX
J2 12 1 10 JX
R2 6 9 100.0E3
RD1 4 11 3.536E3
RD2 4 12 3.536E3
RO1 8 5 150
RO2 7 99 150
RP 3 4 2.143E3
RSS 10 99 1.026E6
VB 9 0 DC 0
VC 3 53 DC 2.200
VE 54 4 DC 2.200
VLIM 7 8 DC 0
VLP 91 0 DC 25
VLN 0 92 DC 25
.MODEL DX D(IS=800.0E-18)
.MODEL JX PJF(IS=15.00E-12 BETA=270.1E-6 VTO=-1)
.ENDS TL071
.TRAN 0 0.5m UIC
.PROBE
.END
```

# Georgia Institute of Technology

## School of Electrical and Computer Engineering

ECE 3043

Electrical and Electronic Circuits Laboratory

Verification Sheet

NAME: \_\_\_\_\_

SECTION: \_\_\_\_\_

AD LOGIN: \_\_\_\_\_

### Experiment 10: Relaxation Oscillators

Procedure	Time Completed	Date Completed	Verification (Must demonstrate circuit)	Points Possible	Points Received
1. Single Op Amp				25	
2. Triangular Wave				25	
3. Inverter				25	
<b>4. 555</b>				25	

Enter your critical frequency below:

$f_{crit}$	
------------	--

To be permitted to complete the experiment during the open lab hours, you must complete at least **four** procedures during your scheduled lab period or spend your entire scheduled lab session attempting to do so. A signature below by your lab instructor, Dr. Brewer, or Dr. Robinson permits you to attend the open lab hours to complete the experiment and receive full credit on the report. Without this signature, you may use the open lab to perform the experiment at a 50% penalty.

SIGNATURE: \_\_\_\_\_

DATE: \_\_\_\_\_



## **ECE 3043 Check-off Requirements for Experiment 10**

Make sure you have made all required measurements before requesting a check-off. For all check-offs, you must demonstrate the circuit or measurement to a lab instructor. All screen captures must have a time/date stamp.

- ✓ For all oscillators: a screen capture of the output showing the peak to peak amplitude and the frequency of oscillation.
- ✓ Comparison the measured frequency of oscillation to the design value. Adjust the circuit component values if the measured value is not within 10% of the design value.